
Lecture5: Small-signal analysis

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

A simple math

- Taylor series expansion
 - Consider a function, $f(x)$.
 - Then, at $x_0 + \Delta x$ (Δx is small.), the function value would be similar to that at x_0 :

$$f(x_0 + \Delta x) \approx f(x_0)$$


- A better approximation?

$$f(x_0 + \Delta x) \approx f(x_0) + \left. \frac{df(x)}{dx} \right|_{x=x_0} \Delta x$$



- Nonlinear function → linearly approximated!

Nonlinear system

- A diode: Input V_D , output I_D


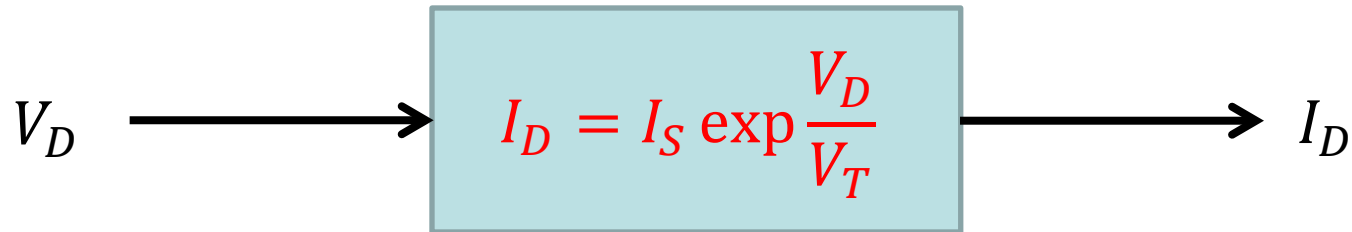


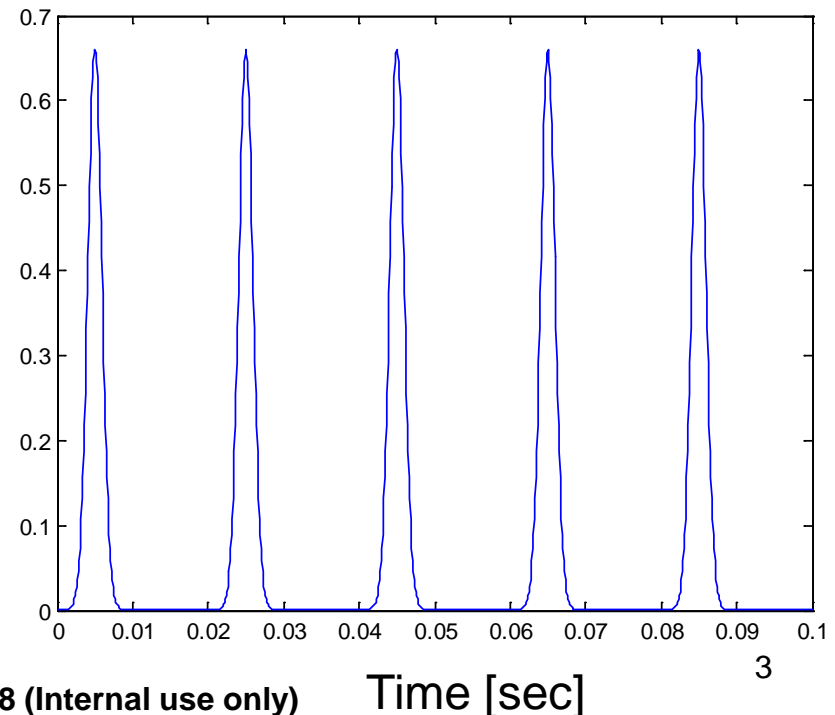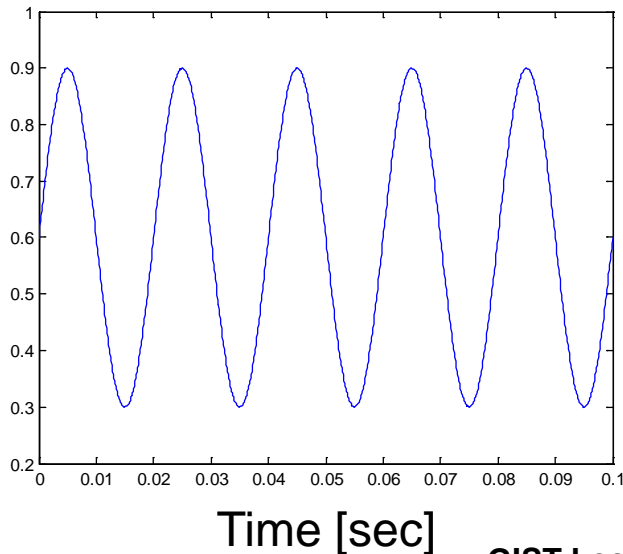- When $V_{in} = 0.6 + 0.3 \sin 2\pi f t$,
 - I_D is not sinusoidal.




Smaller amplitude of input

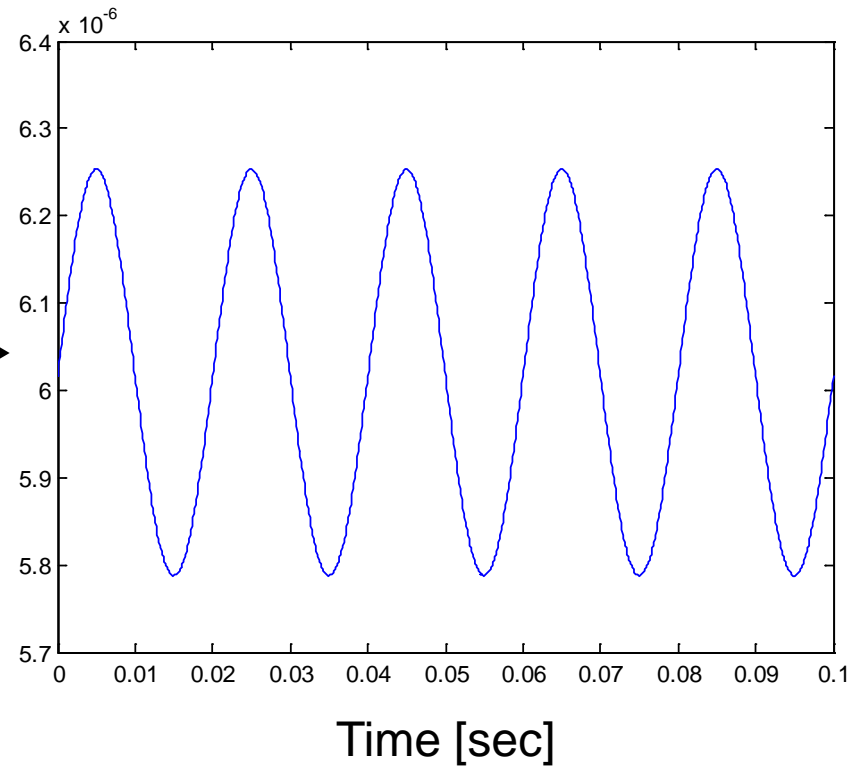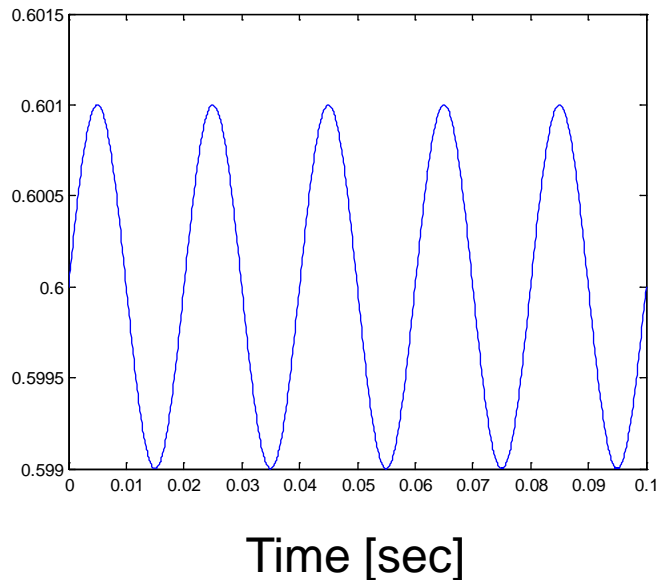- When $V_{in} = 0.6 + 0.001 \sin 2\pi f t$,
 - I_D is almost sinusoidal.



Small-signal analysis


- General case

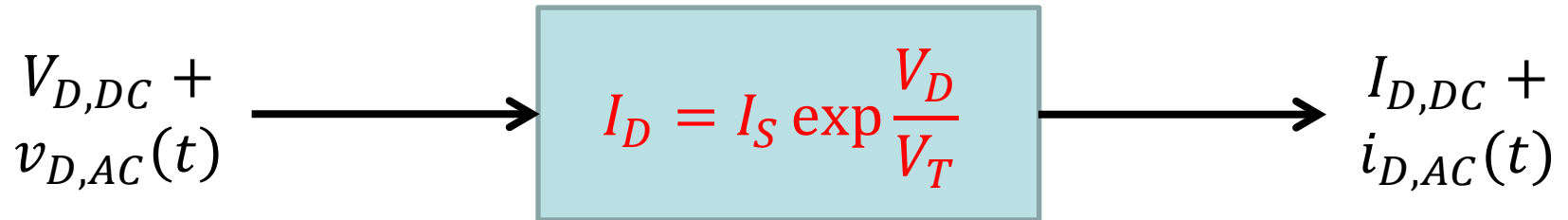

- “Small-signal” case

– When $v_{D,AC}(t)$ is small, then, the AC current is given by

$$i_{D,AC}(t) \approx I_{D,DC} \frac{v_{D,AC}(t)}{V_T}$$

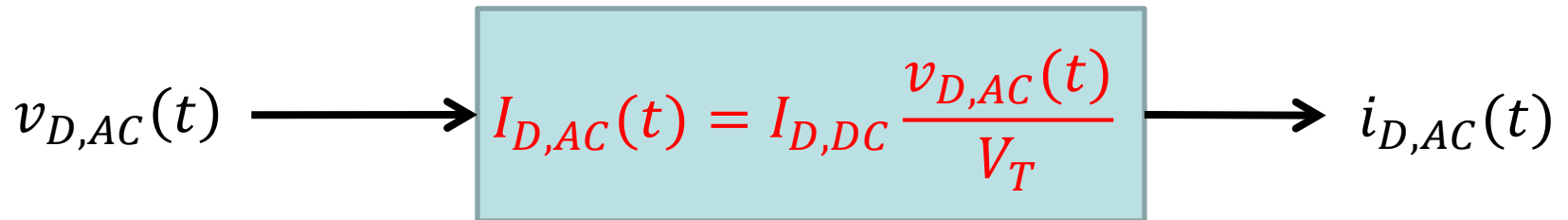

Example 3.18 (Razavi)

- A diode is biased at a current of 1 mA.
 - Determine the current change if V_D changes by 1 mV.

$$\Delta I_D = \frac{I_D}{V_T} \Delta V_D \approx 40 \mu\text{A}$$

- Small-signal resistance
 - As far as small changes in the diode current and voltage are concerned, the device behaves as a linear resistor.

$$r_d = \frac{V_T}{I_D}$$

Example 3.19 (Razavi)

- When the small change in the diode voltage is time-varying,
 - What happens?

$$I_{D2} = I_s \exp \frac{V_{D1} + \Delta V}{V_T} = I_s \exp \frac{V_{D1}}{V_T} \exp \frac{\Delta V}{V_T}$$

$$I_{D2} \approx I_{D1} \left(1 + \frac{\Delta V}{V_T} \right)$$

$$I_{D2} = I_s \exp \frac{V_{D1} + \Delta V \cos \omega t}{V_T} = I_s \exp \frac{V_{D1}}{V_T} \exp \frac{\Delta V \cos \omega t}{V_T}$$

$$I_{D2} \approx I_{D1} \left(1 + \frac{\Delta V \cos \omega t}{V_T} \right)$$

- The output current has the same frequency!