

---

# Lecture4: Diode circuits

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology


# PN junction as a diode

---

- Exponential model

$$I_D = I_s \left( \exp \frac{V_D}{V_T} - 1 \right)$$

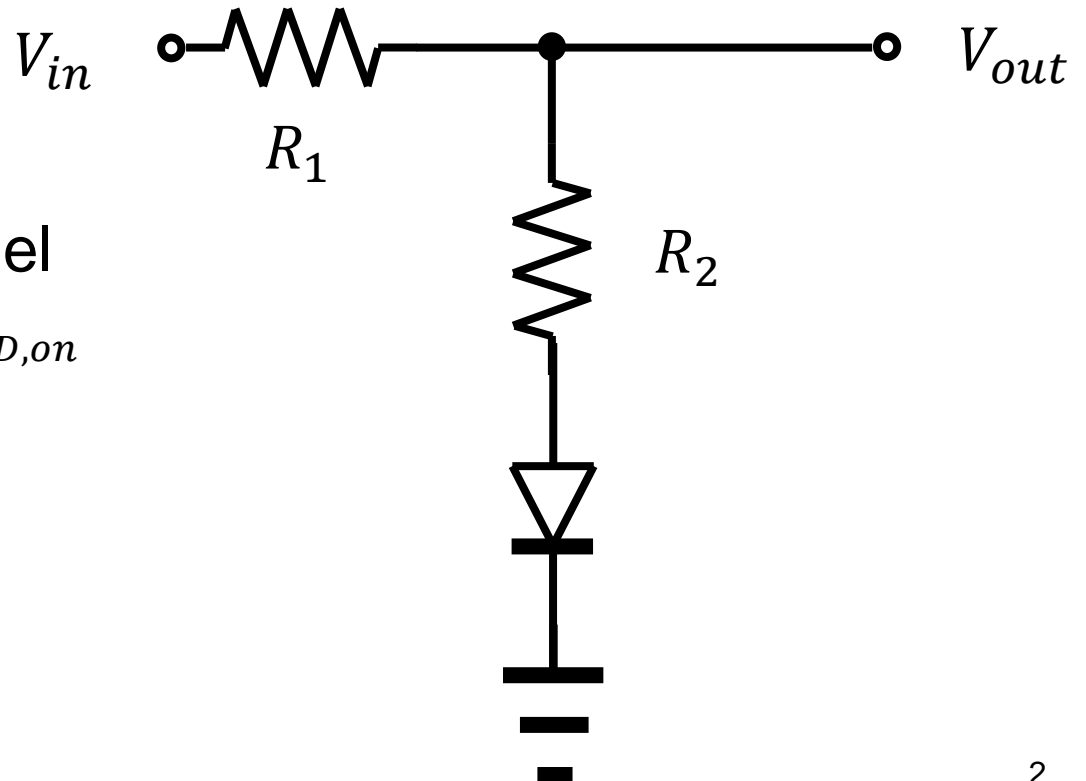
- Constant-voltage model
  - An “offset” voltage of  $V_{D,on}$


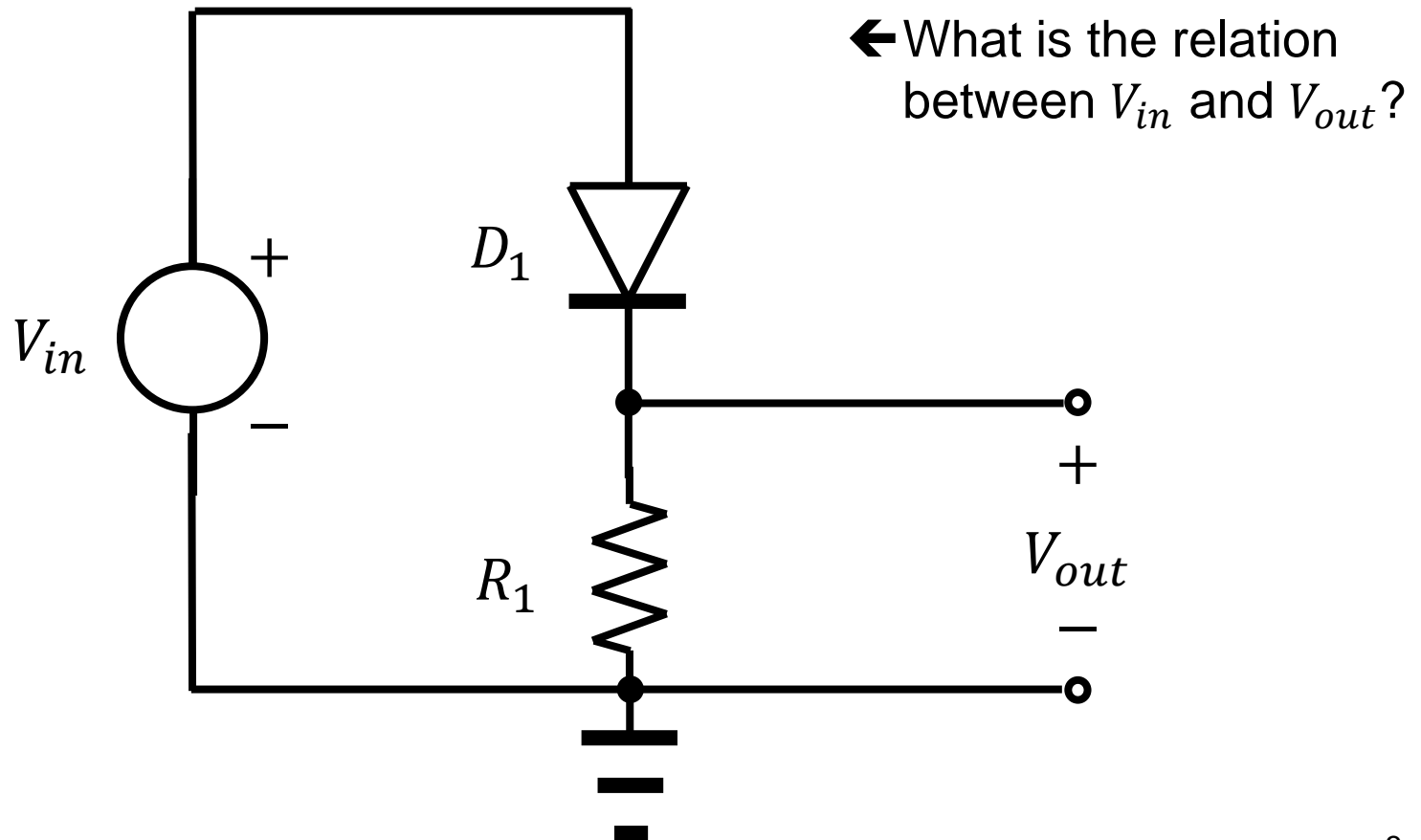
# Rectifier



---

- Revisiting our first example
  - Analyze it by using the constant-voltage model


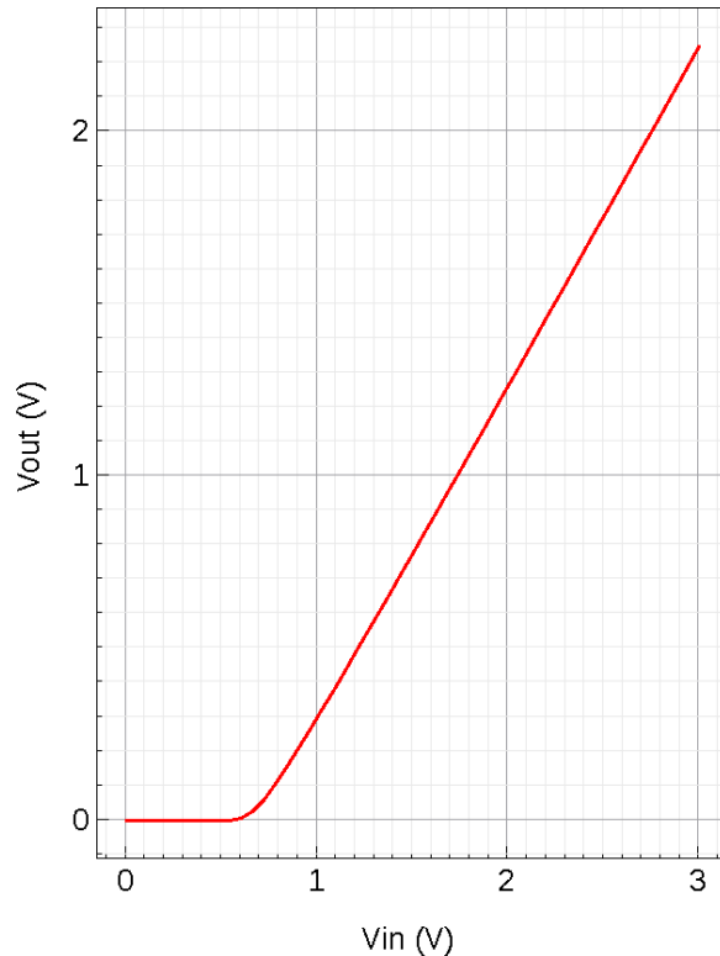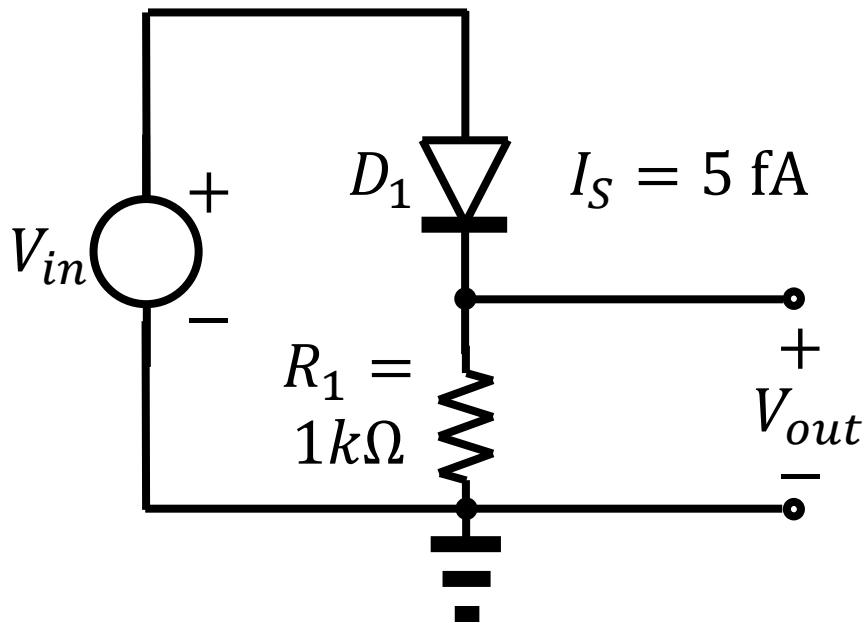
# Simulation result


- Specific example of  $I_S = 5 \text{ fA}$  and  $R_1 = 1 \text{ k}\Omega$ .


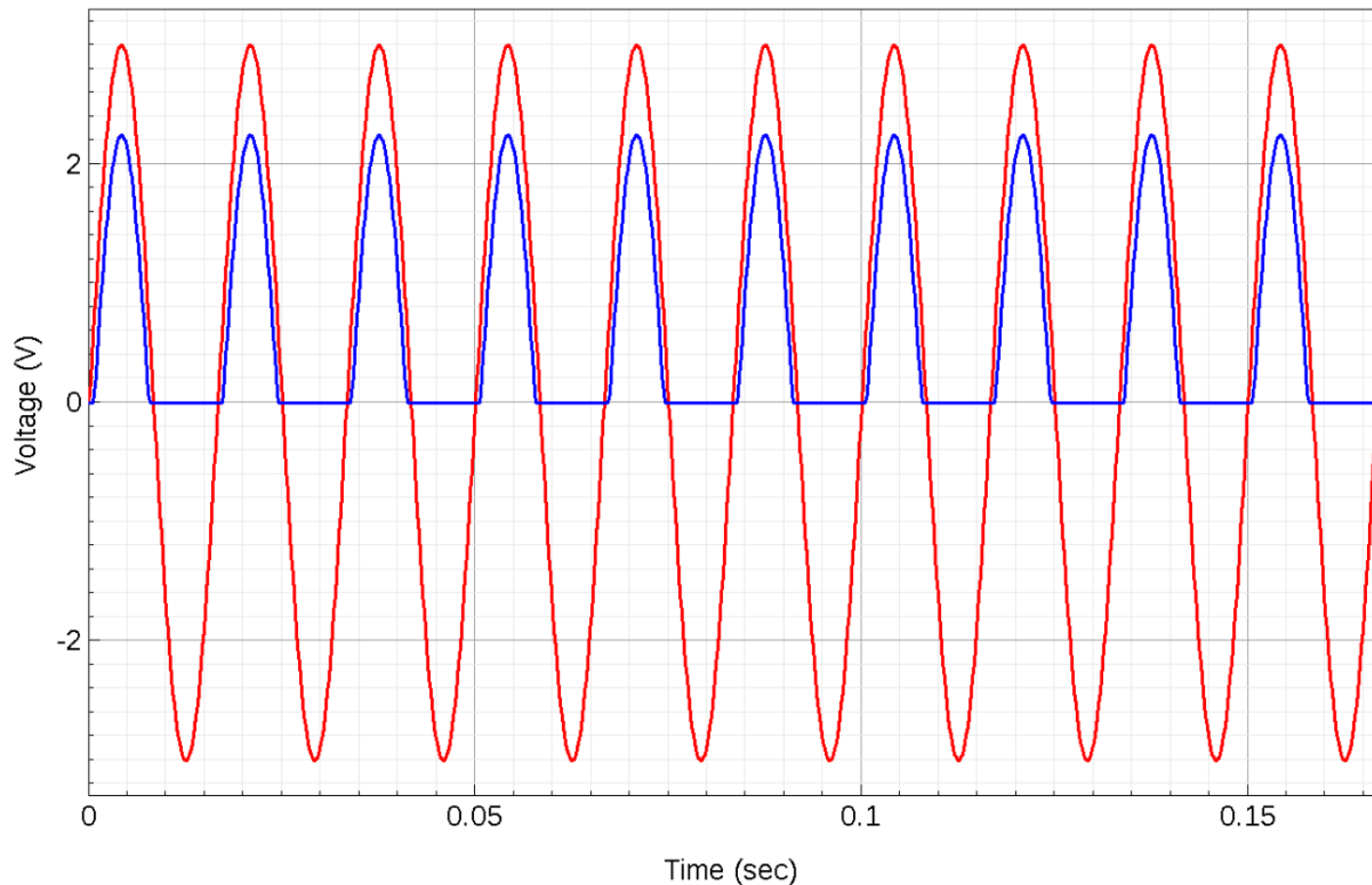
# Time-varying voltage source

---


- For example,  $V_{in}(t) = 3 \sin(2\pi ft)$  V.
  - 60 Hz, 10 periods


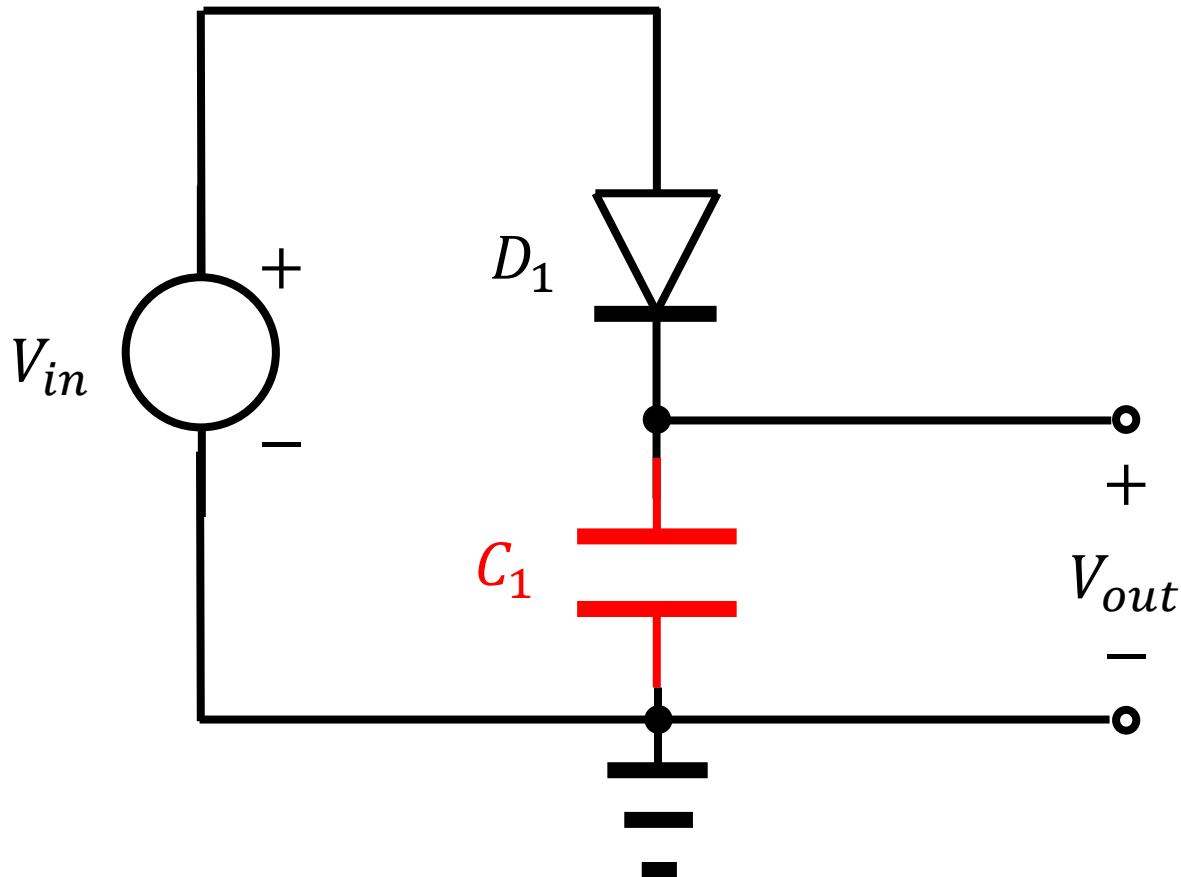
# Introducing a capacitor

---

- Difference from the previous one?
  - First, consider the DC case. Remember that  $I_C = C_1 \frac{d}{dt} V_{out}$ .



# Qualitative understanding


---

- Consider the first period.
  - When the input voltage exceeds  $V_{D,on}$ , the diode is turned on.
  - The charge is stored in the capacitor. Hence, the output voltage increases.
  - When the input voltage is lower than  $V_{D,on}$ , the output voltage does not change. (*Why?*)
- After the first period...
  - In the second period, the diode current is smaller than the one in the first period. (*Why?*)
  - After some periods, the diode current vanishes.
  - A DC output voltage is established.
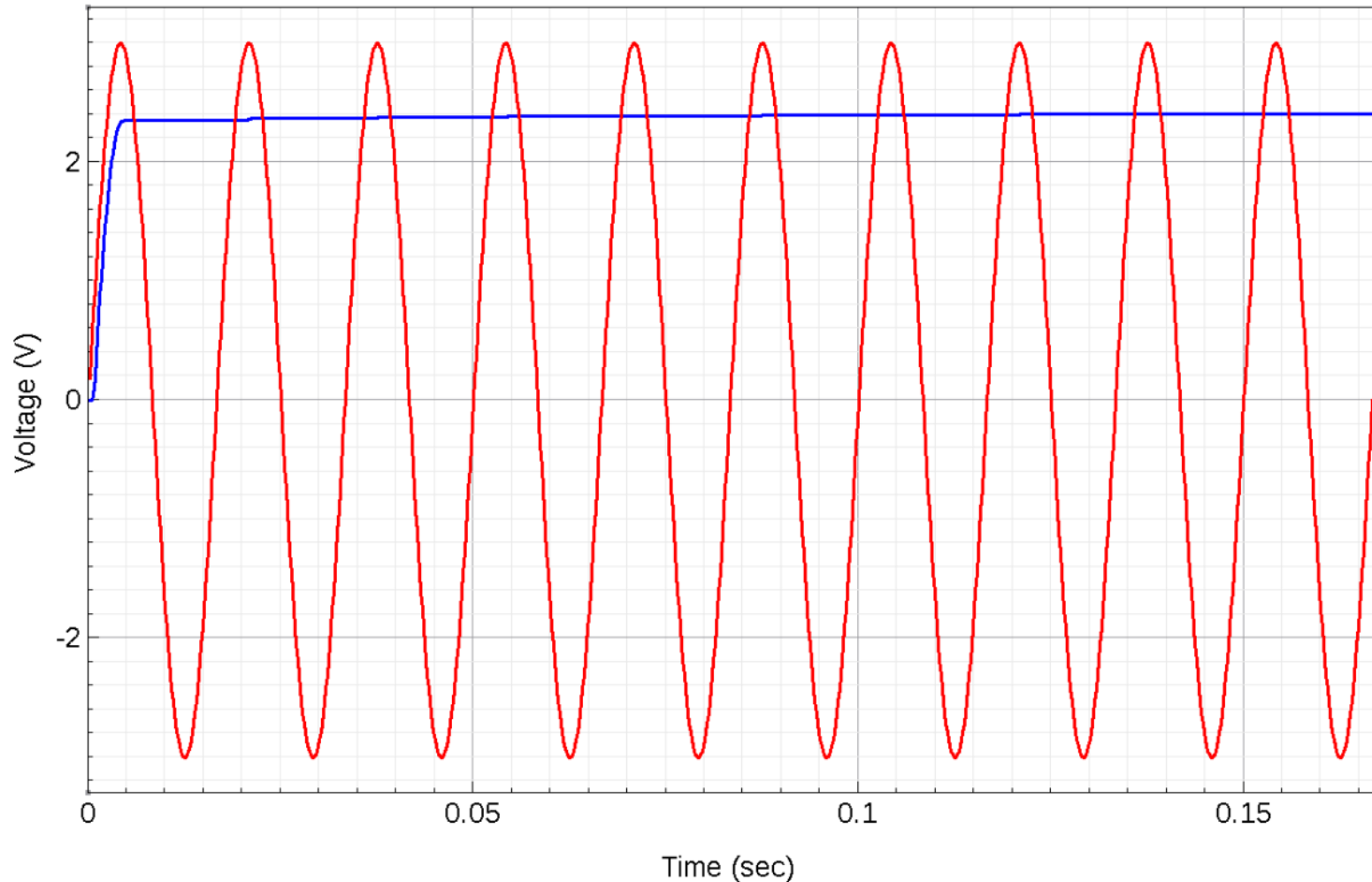
# Simulation result

---

- The capacitance,  $C_1 = 1\ \mu\text{F}$ .






# Example 3.6 (Razavi)

---


- An OR gate

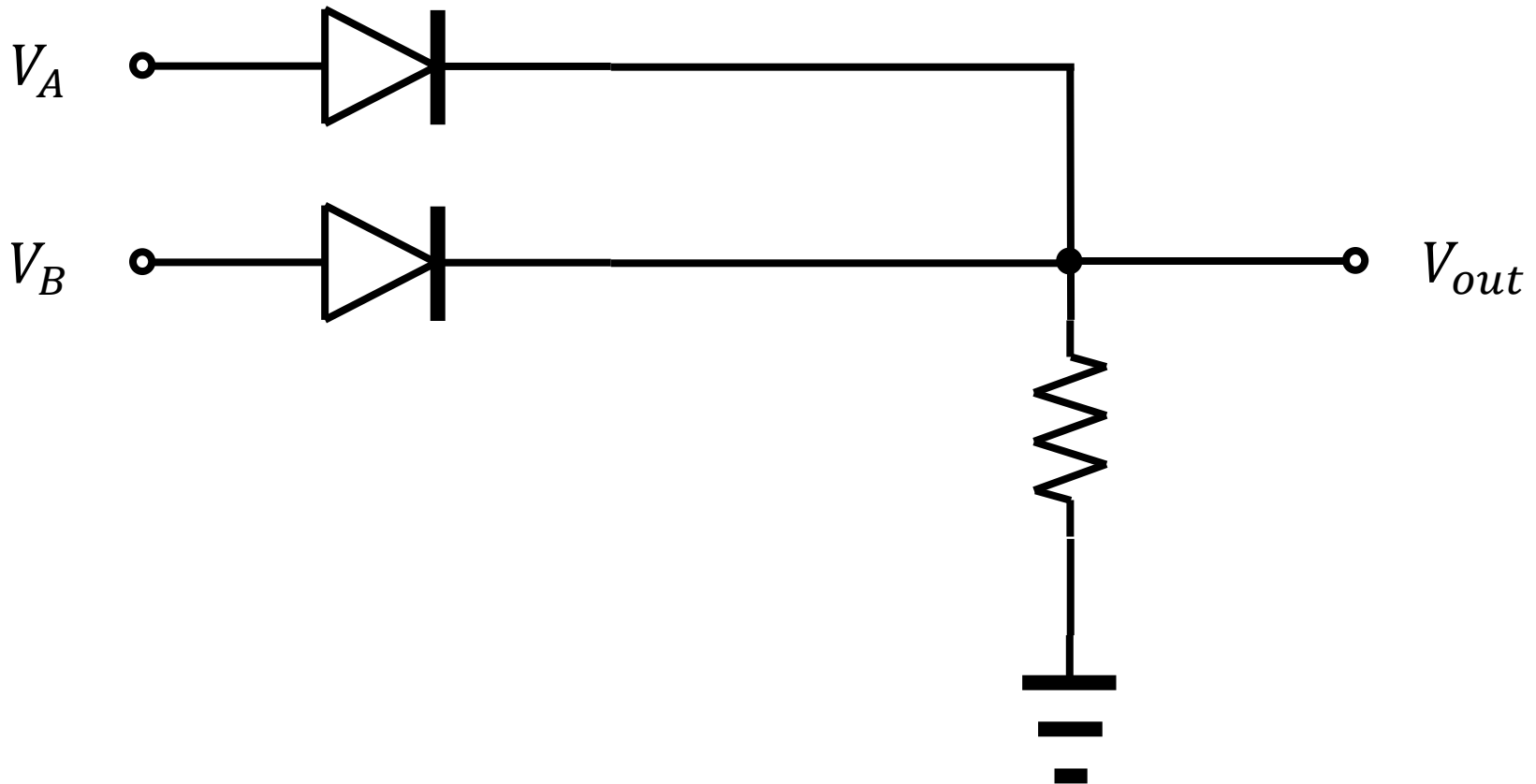

# Limiter

---

- Level-shift for both half cycles

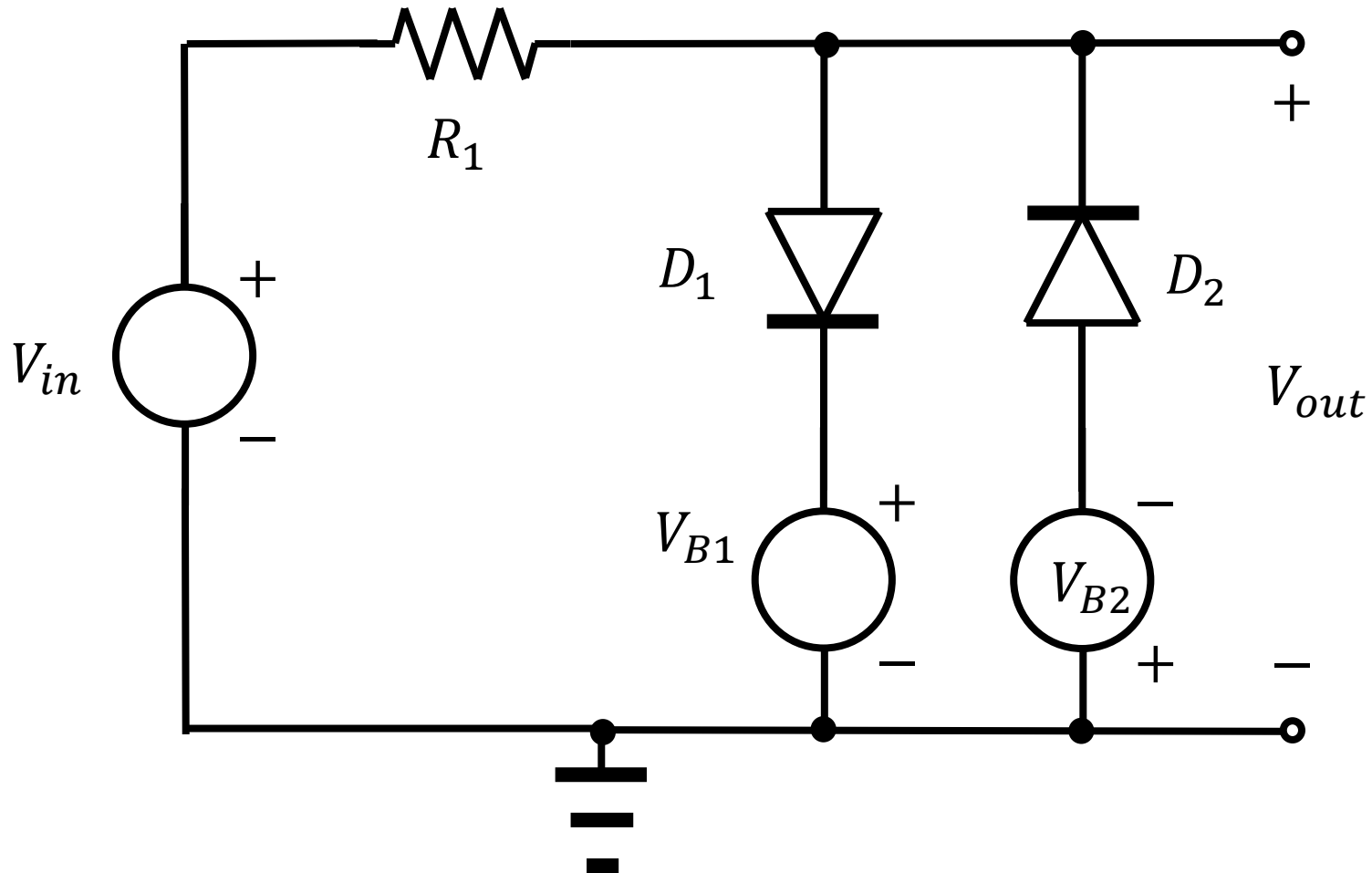

# A simple math, again

---

- Taylor series expansion
  - Consider a function,  $f(x)$ .
  - Then, at  $x_0 + \Delta x$  ( $\Delta x$  is small.), the function value would be similar to that at  $x_0$ :

$$f(x_0 + \Delta x) \approx f(x_0)$$


- A better approximation?

$$f(x_0 + \Delta x) \approx f(x_0) + \left. \frac{df(x)}{dx} \right|_{x=x_0} \Delta x$$



- Nonlinear function → linearly approximated!
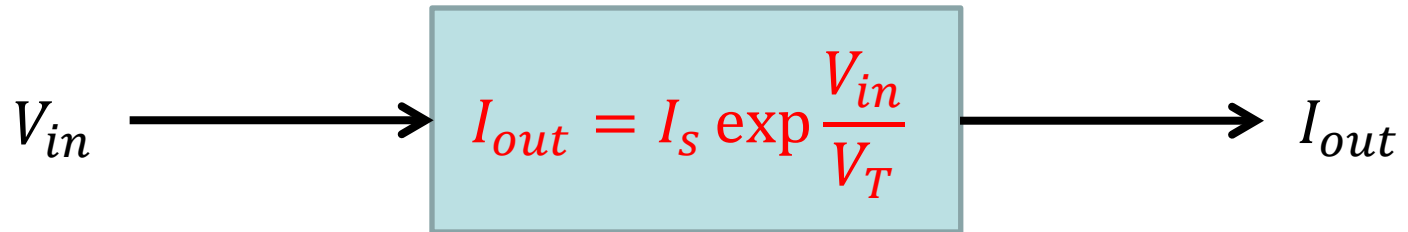
# A system

- A system (You know what it actually represents.)



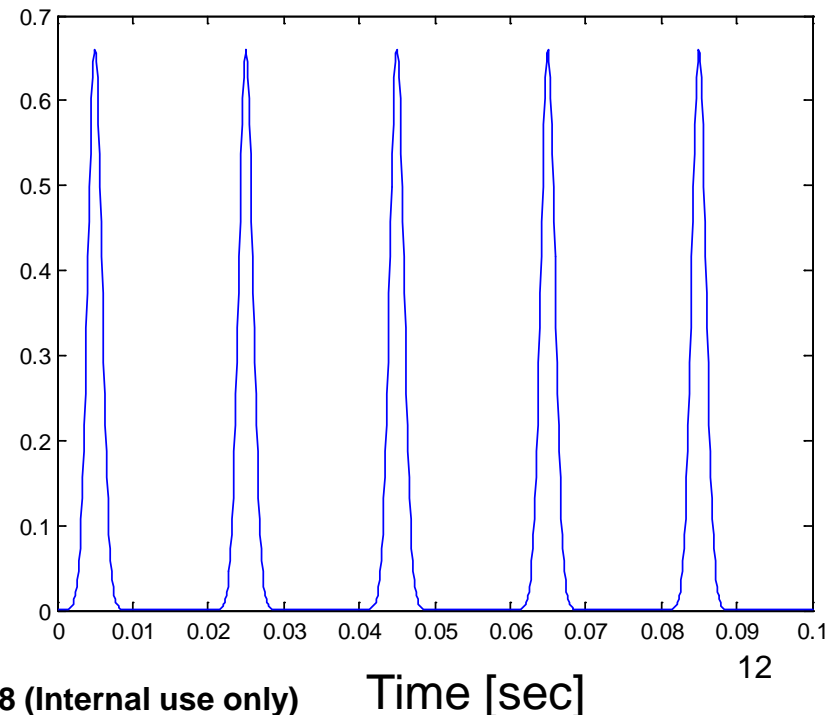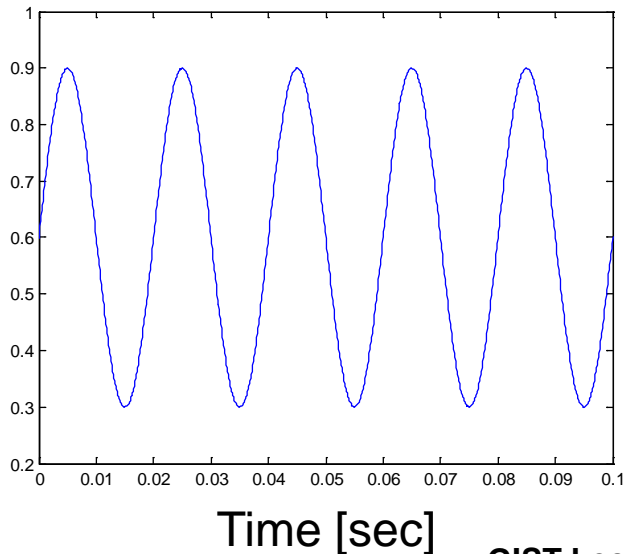- When  $V_{in} = 0.6 + 0.3 \sin 2\pi f t$ ,
  - Certainly, nonlinear!



# Smaller amplitude?

---

- When  $V_{in} = 0.6 + 0.001 \sin 2\pi f t$ ,
  - Nonlinear?

