

---

# Lecture12:

# CMOS amplifier, biasing


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
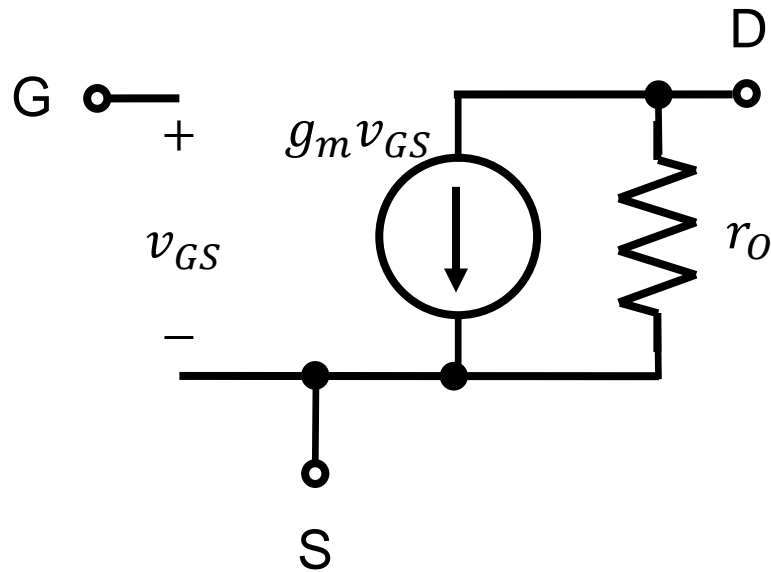
# Summary

---

- Small-signal MOSFET model
  - Two branches are related with two partial derivatives.



# Impedances


---

- Resistance,  $V(t) = R I(t)$ 
  - It is assumed that  $V(t)$  and  $I(t)$  are in the same phase.
  - Consider  $V(t) = V_0 \sin \omega t$  and  $I(t) = I_0 \cos \omega t$ . Then, what is the resistance?
  - In this case, we can introduce a phasor voltage,  $V(\omega)$ , and a phasor current,  $I(\omega)$ .
  - The relation between  $V(t)$  and  $V(\omega)$  is
$$V(t) = \text{Re}[V(\omega)e^{j\omega t}]$$
  - When  $V(t) = V_0 \sin \omega t$ , the phasor voltage is  $V(\omega) = -jV_0$ .
  - When  $I(t) = I_0 \cos \omega t$ , the phasor voltage is  $I(\omega) = I_0$ .
- Impedance,  $V(\omega) = Z(\omega)I(\omega)$ 
  - In the above example,  $Z(\omega) = -j \frac{V_0}{I_0}$ . A purely imaginary number.
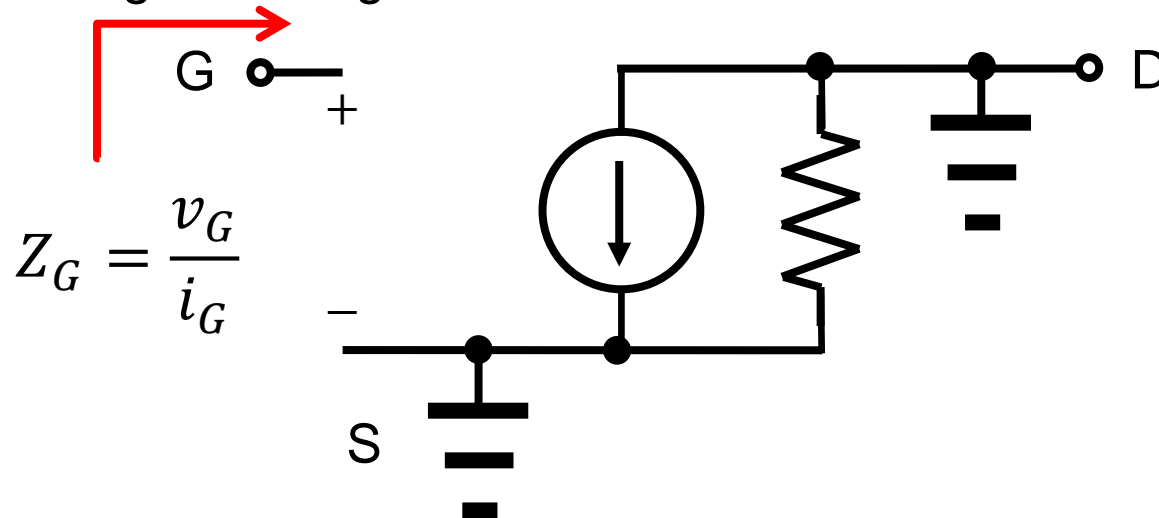
# Impedances of MOSFET

---

- “Looking into the TERMINAL,” we see the impedance of the TERMINAL.
  - Consider the following cases:
  - 1) Looking into the gate. The source and drain are ac-grounded.





- 2) Looking into the drain. The source and gate are ac-grounded.
- 3) Looking into the source. The gate and drain are ac-grounded.
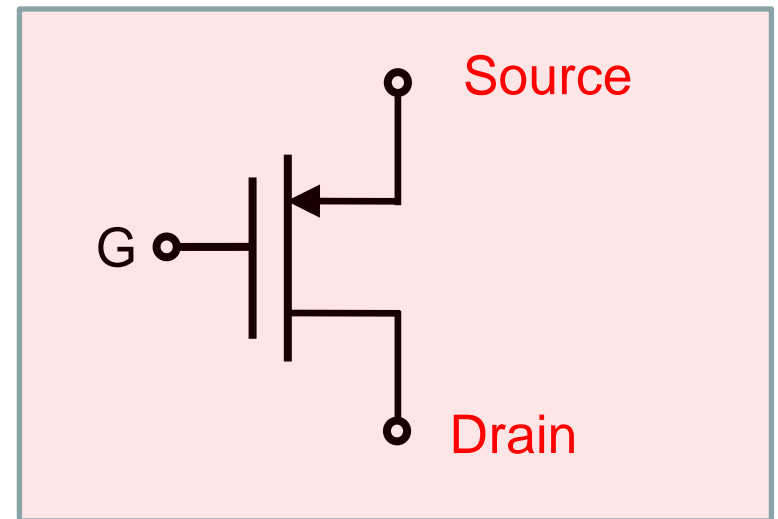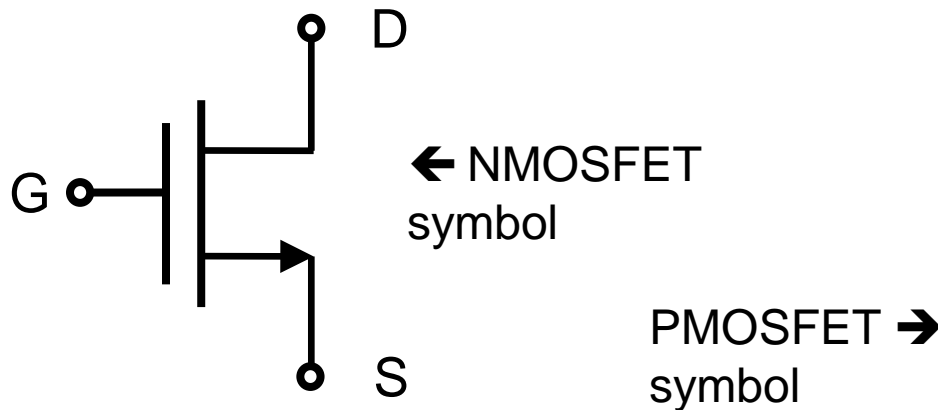
# CMOS

---

- 9's complementary of 123?
  - 876
- Complementary MOS
  - Here we have an NMOSFET.
  - A device where the transport is dominated by holes.




- Why is it important?
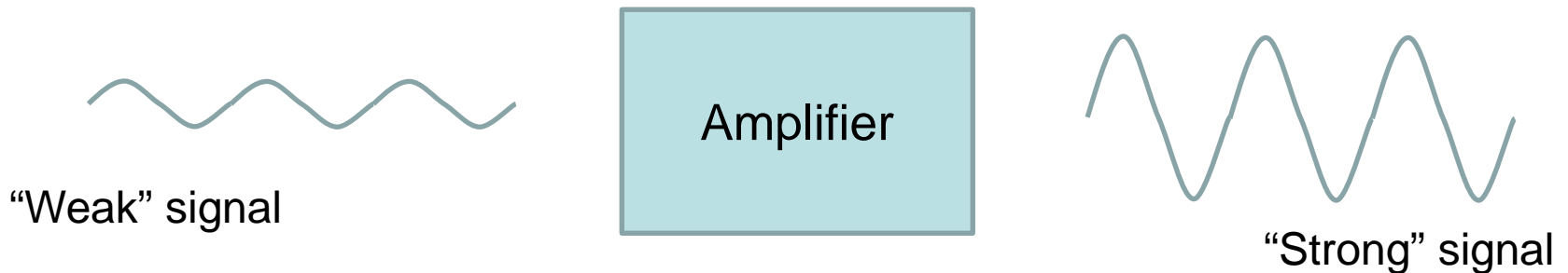
# Why amplifiers?

---

- Signal amplification
  - Usually, signals are “weak.” (in the  $\mu\text{V}$  or  $\text{mV}$  range)
  - It is too small for reliable processing.
  - If the signal magnitude is made larger, processing is much easier.




- Desirable properties
  - Low power consumption
  - High speed operation
  - Low noise
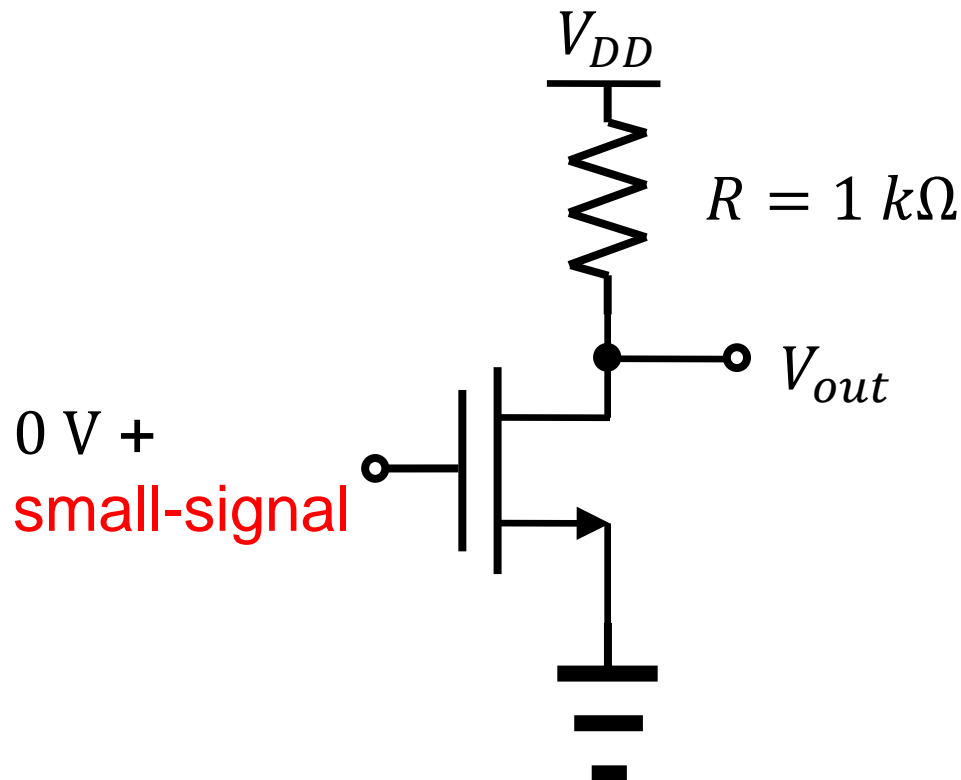
# Transistor turned off

---


- The example 17.5 shows an amplifier circuit.
  - But, the transistor is not turned on.
  - The circuit generates no output signal.


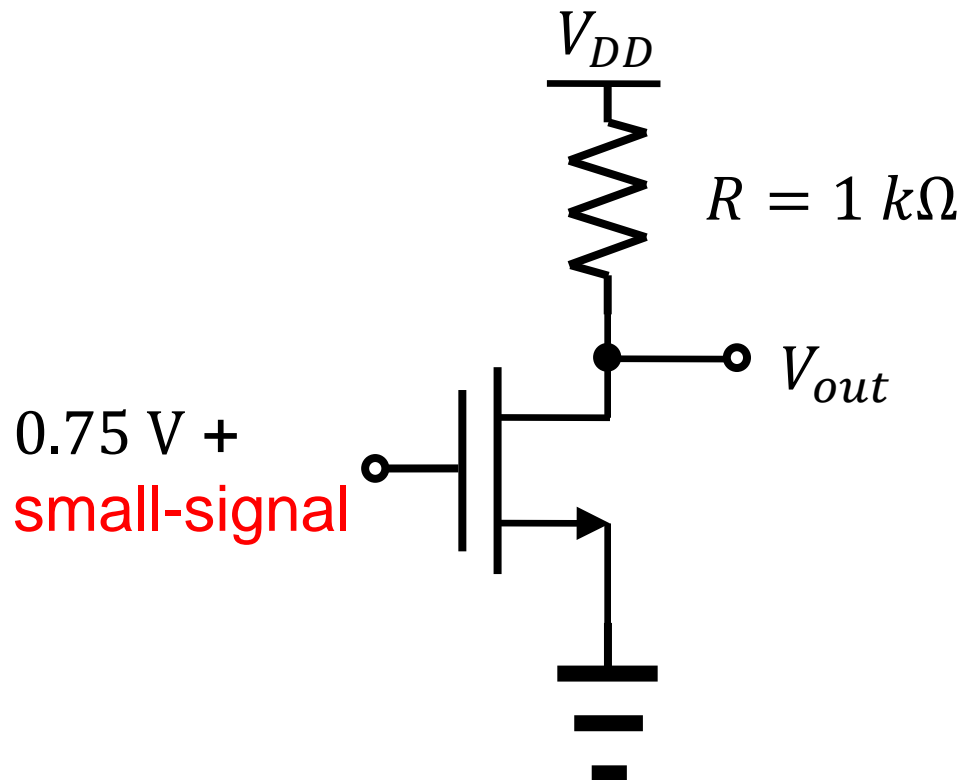
# This is a solution.

---

- The example 17.7 shows a revised circuit.
  - Then, how can we generate 0.75 V, for example?
  - Use of a separate battery can be a way.





# Simple biasing (1/2)

---


- A better way

- The gate bias voltage is

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD} \quad (17.10)$$

- The drain current is
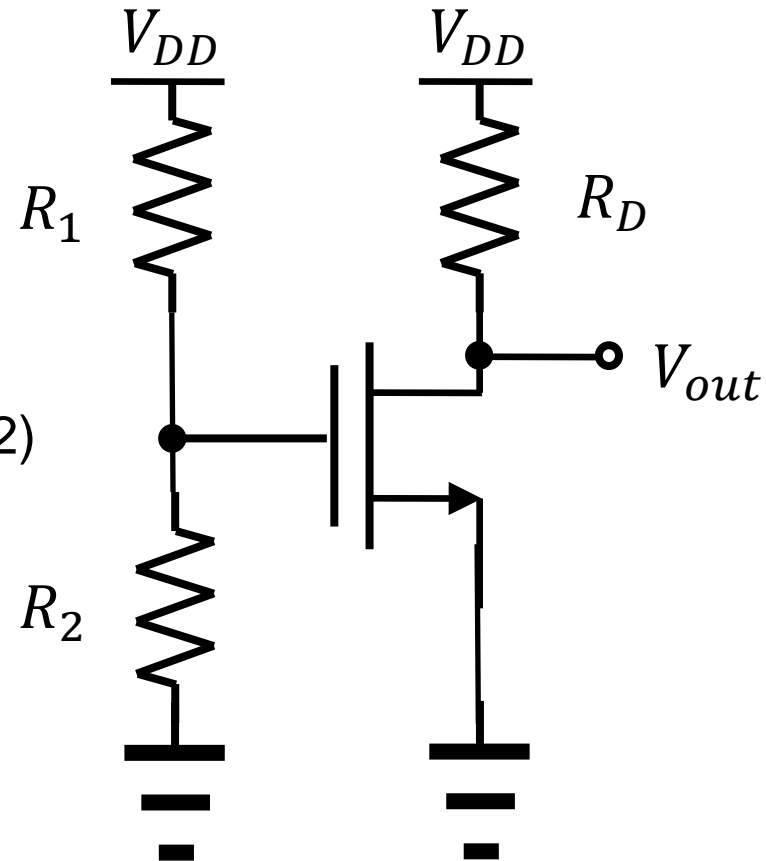
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2 \quad (17.12)$$



# Simple biasing (2/2)

---

- How to apply the small-signal input
  - Use a capacitor!

