

---

# Lecture23:

## Operational amplifier (2)


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
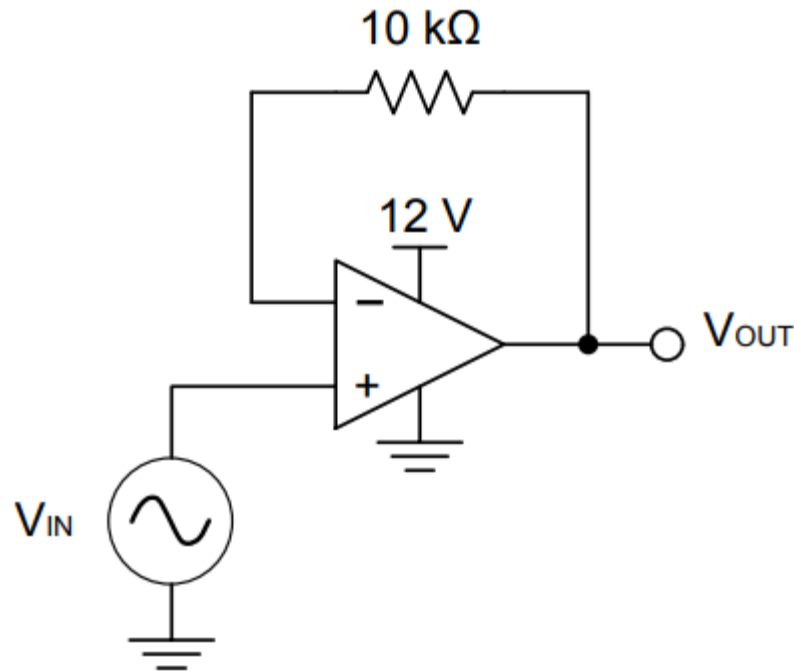
# Unit-gain buffer

---

- Driving a relatively high current load
  - The output resistance of the op amp is almost negligible.
  - So, the resistance can provide as much current as necessary to the output load.




Schematic of a unit-gain buffer (Texas Instruments)
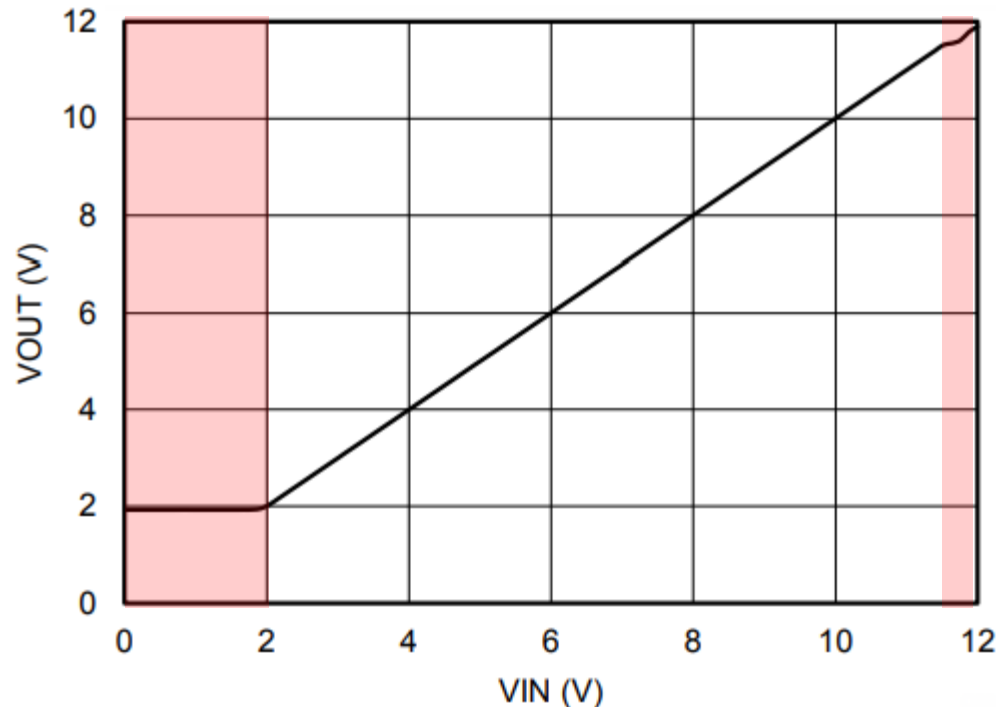
# Its output characteristics

---

- Realistic curve
  - Using a negative voltage on the lower rail (rather than ground) allows the amplifier to maintain linearity for inputs below 2 V.



Output voltage versus input voltage (Texas Instruments)


# Noninverting amplifier (1)

- Calculate the gain.
  - The input resistance of the op amp is large.

$$V_{in2} = \frac{R_2}{R_1 + R_2} V_{out}$$

- Due to the high op amp gain,  
 $V_{in2} \approx V_{in}$

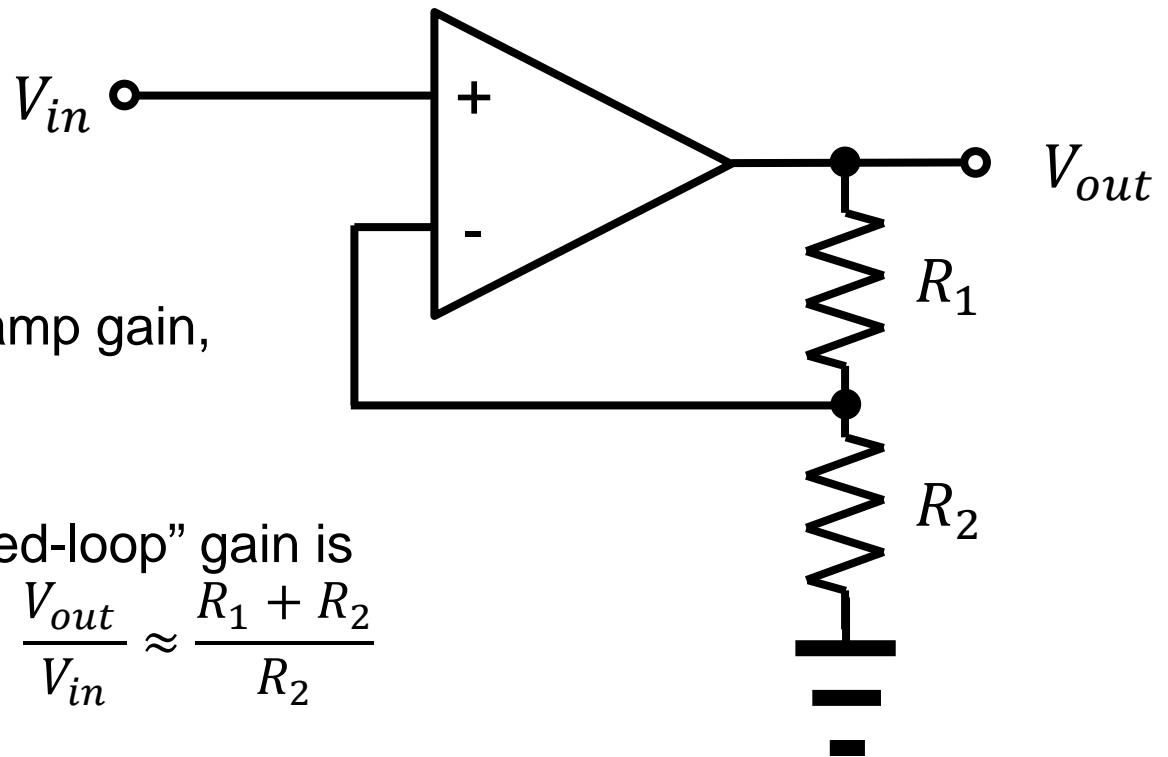- Therefore, the “closed-loop” gain is  
$$\frac{V_{out}}{V_{in}} \approx \frac{R_1 + R_2}{R_2}$$




# Noninverting amplifier (2)

- Repeat it again with a finite  $A_0$ .

- Now,

$$V_{out} = A_0(V_{in} - V_{in2})$$

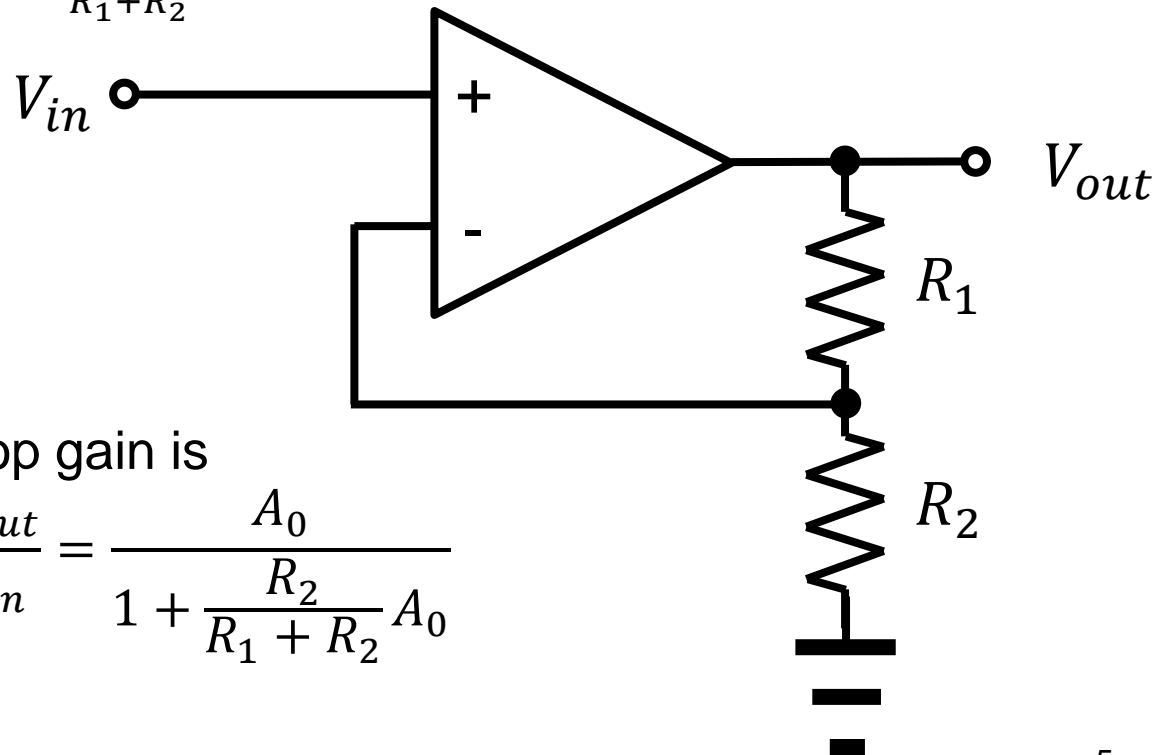- Remember that  $V_{in2} = \frac{R_2}{R_1 + R_2} V_{out}$ .



- Then, the closed-loop gain is

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0}$$

# Inverting amplifier


---

- The inverting input is called a “virtual ground.”

- Then, the output voltage is

$$V_{out} = -R_1 \frac{V_{in}}{R_2}$$

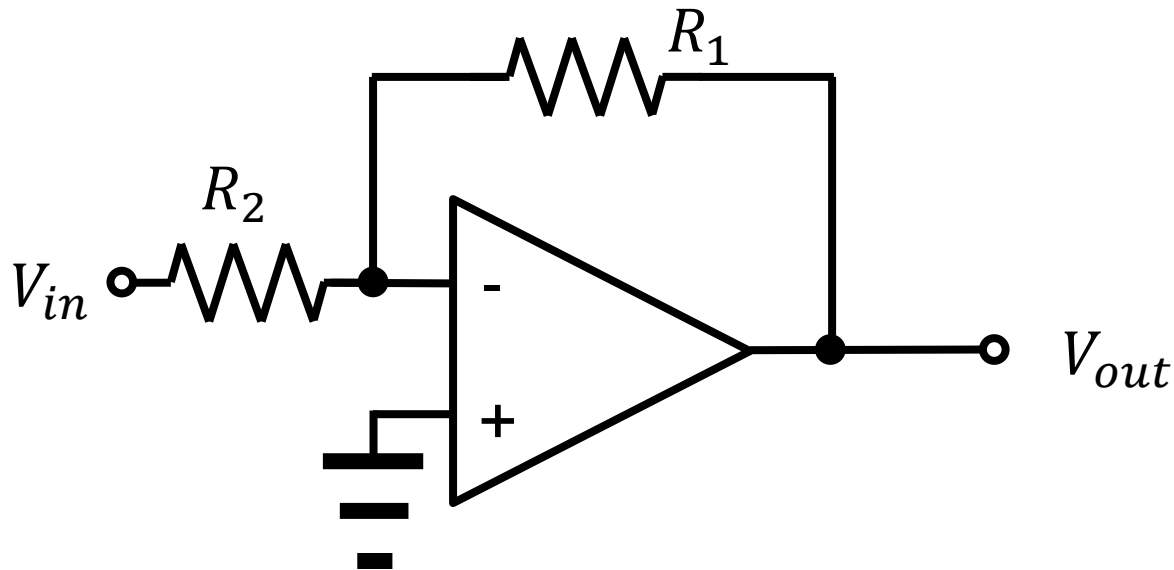- Its input impedance is equal to  $R_2$ .



# Integrator

---

- Instead of a resistor, a capacitor is introduced.
  - In the time domain,

$$\frac{V_1}{R_1} = -C_1 \frac{dV_{out}}{dt}$$

