

---

# Lecture4: Diode circuits

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology


# PN junction as a diode

---

- Exponential model

$$I_D = I_s \left( \exp \frac{V_D}{V_T} - 1 \right)$$

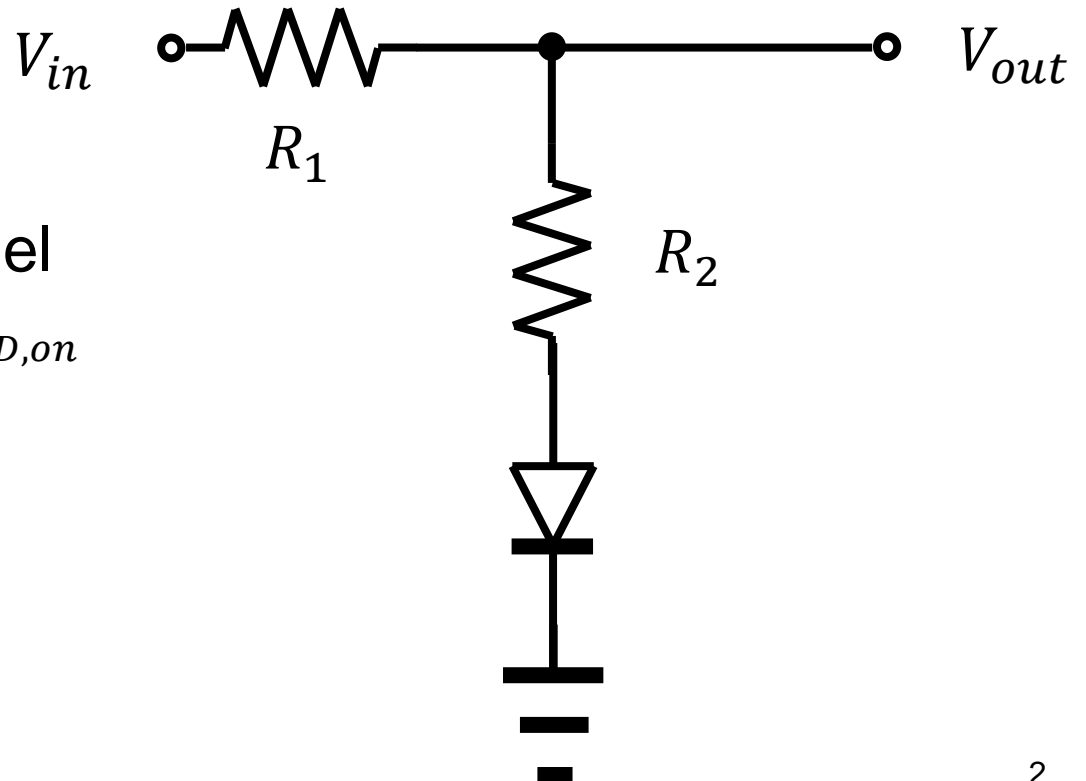
- Constant-voltage model
  - An “offset” voltage of  $V_{D,on}$



# Example 3.6 (Razavi)

---


- An OR gate

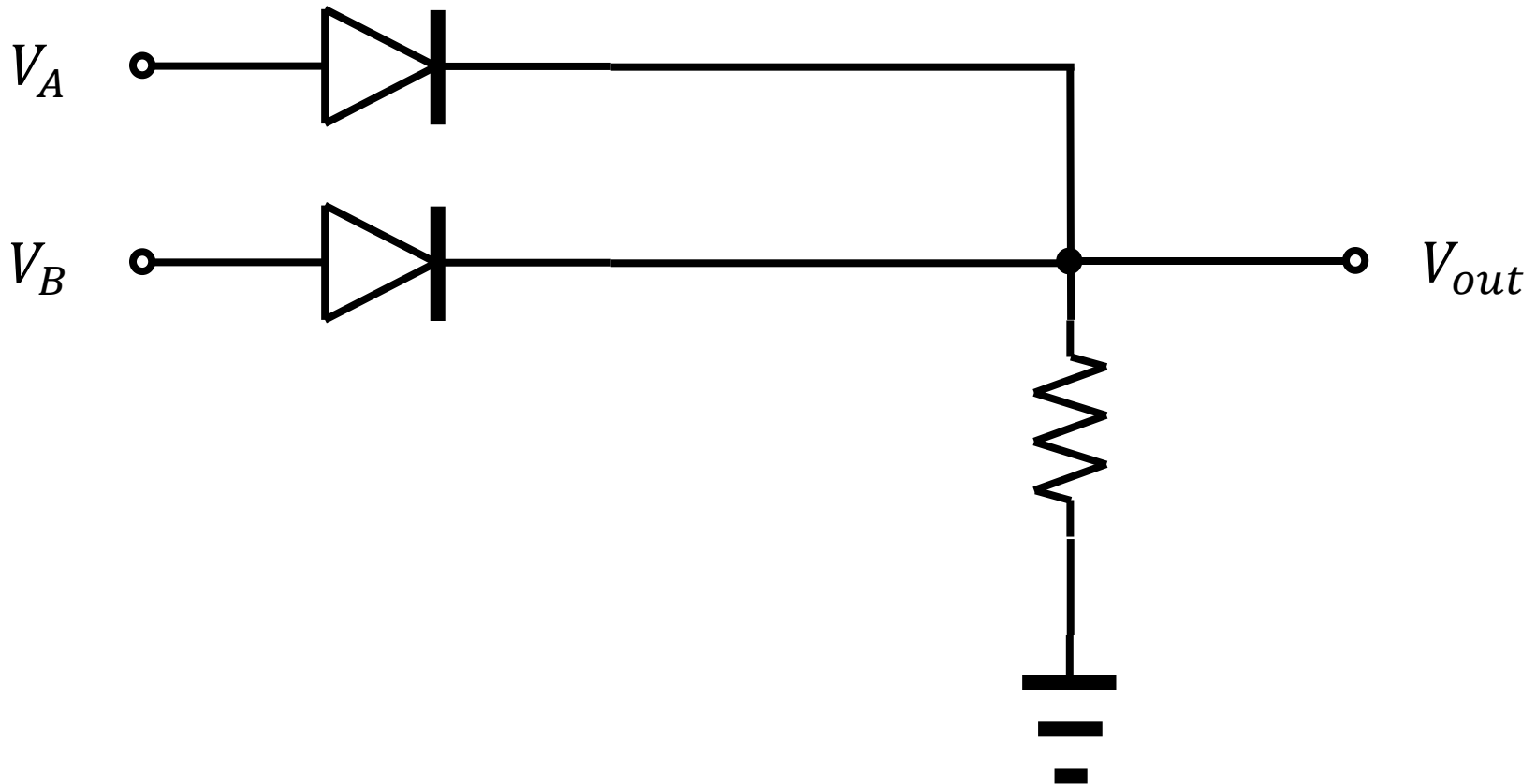

# Rectifier

---


- Revisiting our first example

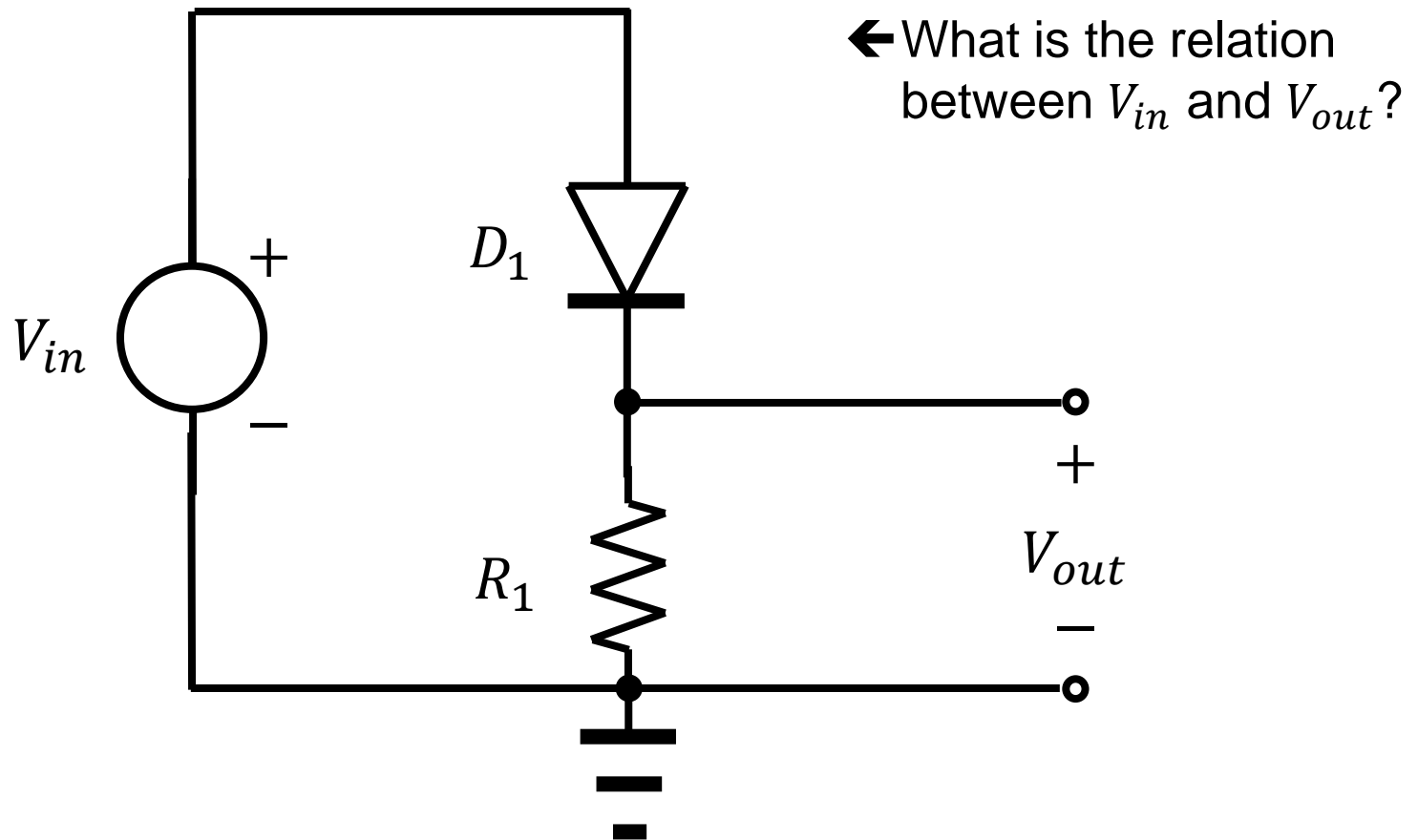

# Introducing a capacitor

---

- Difference from the previous one?

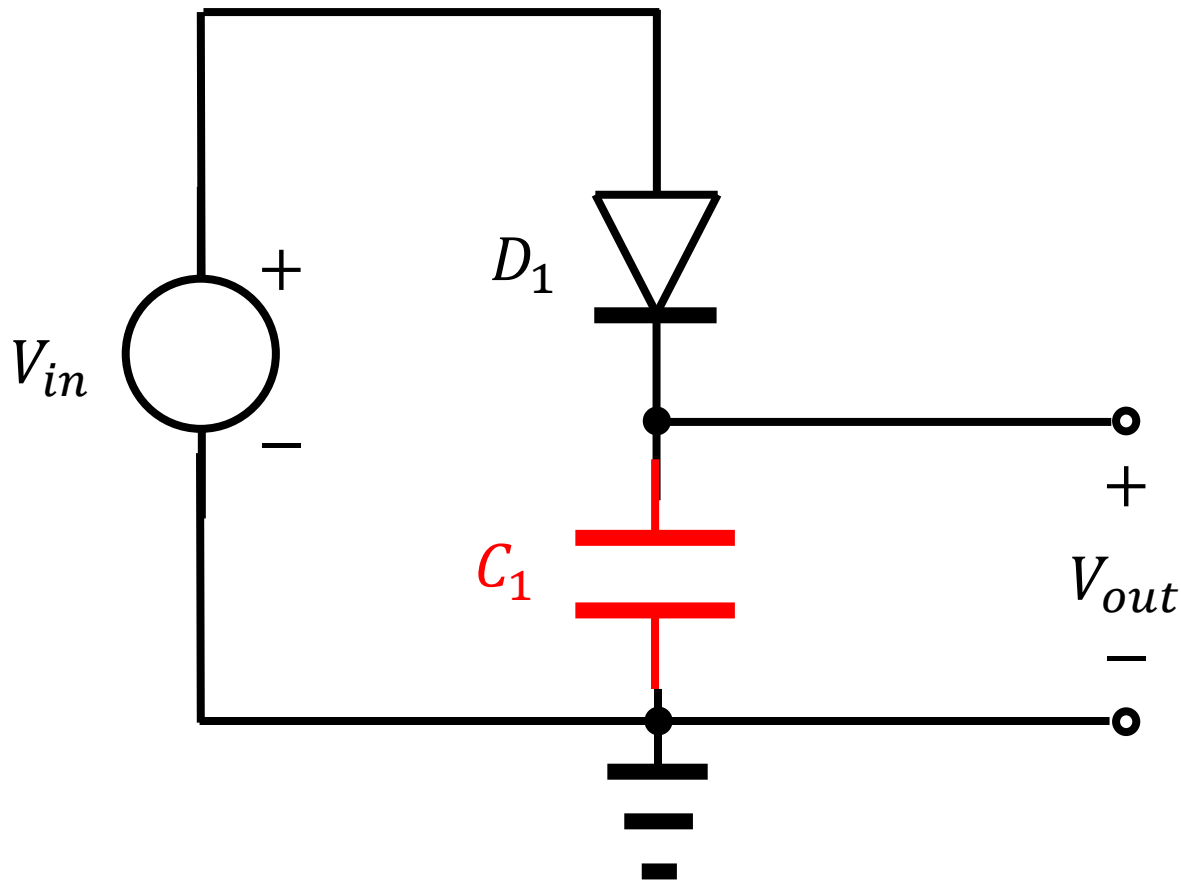


# Introducing a capacitor

---

- Difference from the previous one?


Voltage [V]

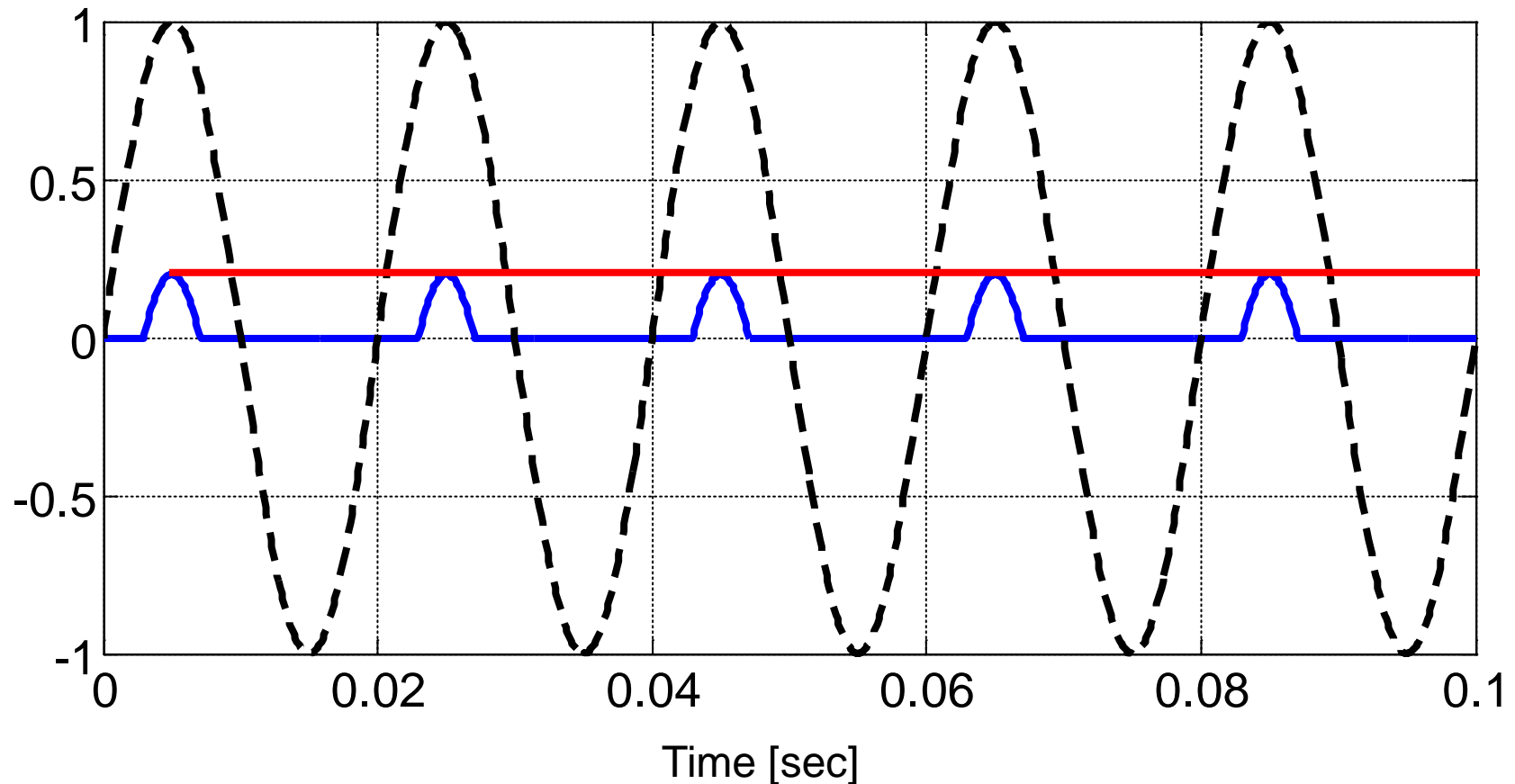

# Limiter

---

- Level-shift for both half cycles

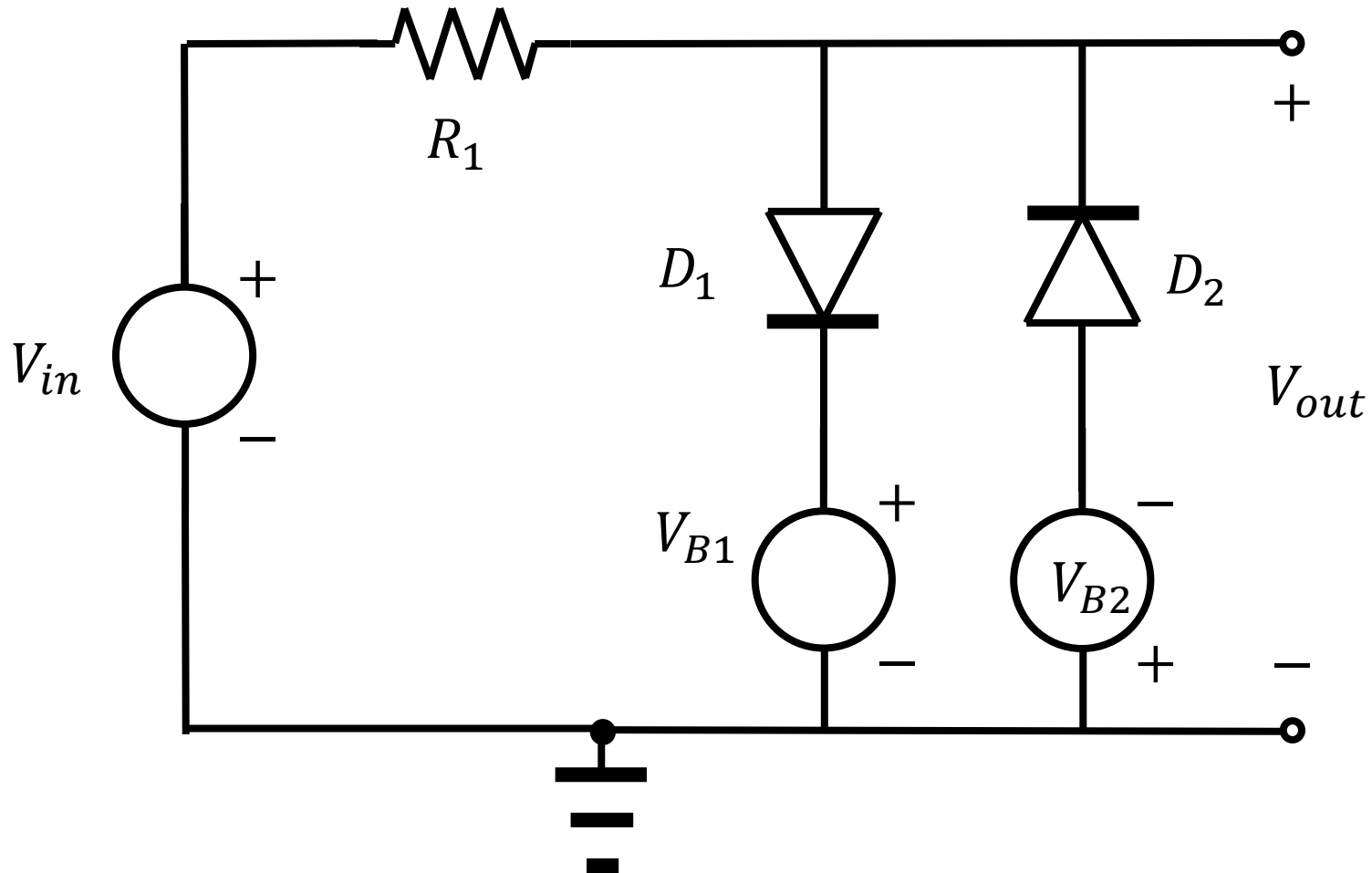

# A simple math, again

---

- Taylor series expansion
  - Consider a function,  $f(x)$ .
  - Then, at  $x_0 + \Delta x$  ( $\Delta x$  is small.), the function value would be similar to that at  $x_0$ :

$$f(x_0 + \Delta x) \approx f(x_0)$$

- A better approximation?


$$f(x_0 + \Delta x) \approx f(x_0) + \left. \frac{df(x)}{dx} \right|_{x=x_0} \Delta x$$

- Nonlinear function → linearly approximated!




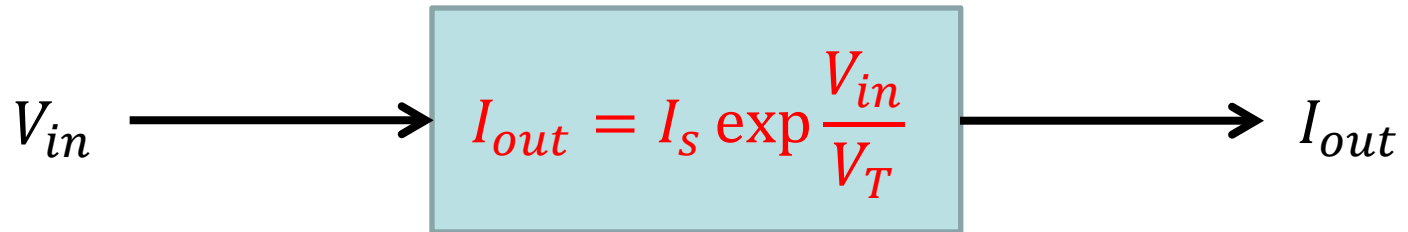
# A system

- A system (You know what it actually represents.)



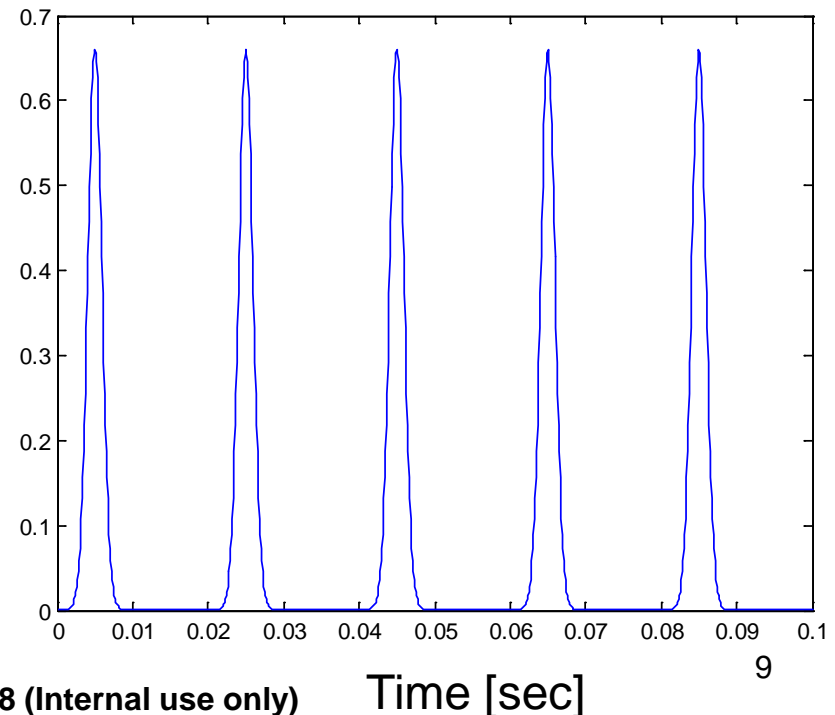
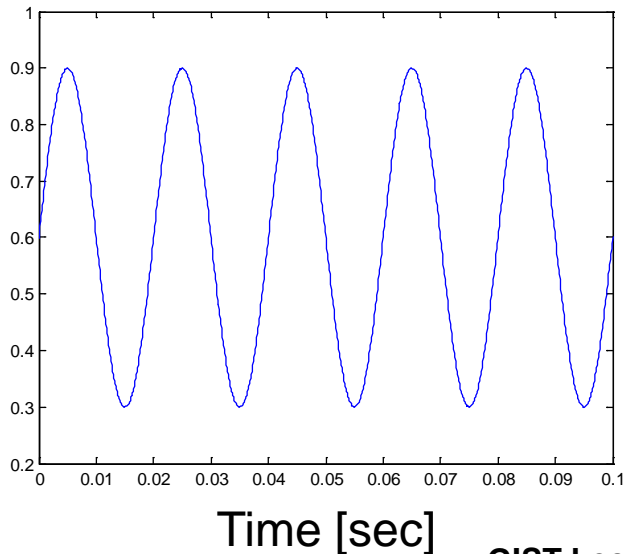
- When  $V_{in} = 0.6 + 0.3 \sin 2\pi f t$ ,
  - Certainly, nonlinear!


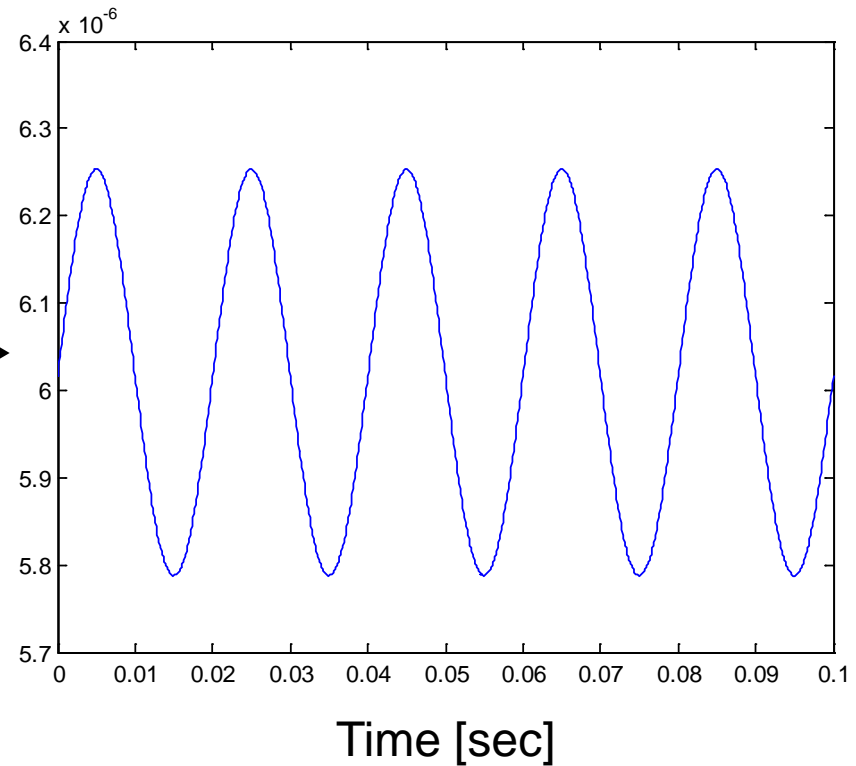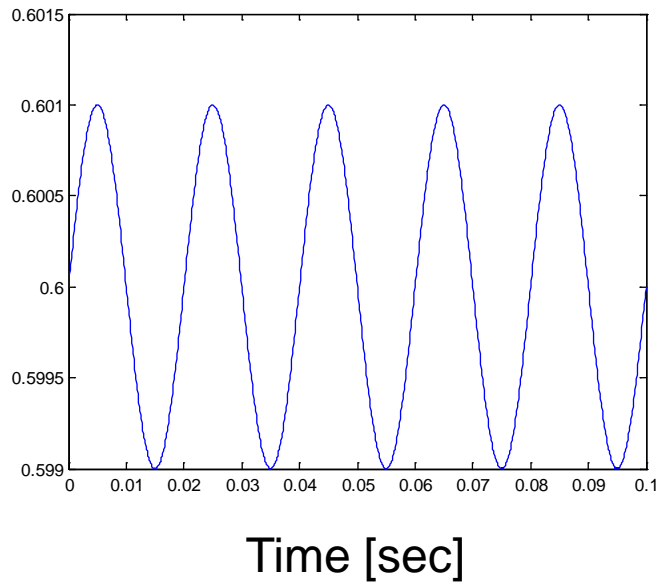
# Smaller amplitude?

---

- When  $V_{in} = 0.6 + 0.001 \sin 2\pi f t$ ,
  - Nonlinear?



# Verbatim (p. 66)

---

- These thought lead us to the extremely important concept of “small-signal operation,” whereby the circuit experiences only small changes in voltages and currents.
- Therefore it can be simplified through the use of “small-signal models” for nonlinear devices.
- The simplicity arises because such models are linear, allowing standard circuit analysis and obviating the need for iteration.

# Exponential

---

- Simple, but important example

- A diode is biased to a voltage  $V_{D1}$ .

- The current is given by  $I_{D1}$ .

$$I_{D2} = I_s \exp \frac{V_{D1} + \Delta V}{V_T} = I_s \exp \frac{V_{D1}}{V_T} \exp \frac{\Delta V}{V_T}$$

$$I_{D2} \approx I_{D1} \left( 1 + \frac{\Delta V}{V_T} \right)$$

# Example 3.18

---

- A diode is biased at a current of 1 mA.
  - Determine the current change if  $V_D$  changes by 1 mV.

$$\Delta I_D = \frac{I_D}{V_T} \Delta V_D \approx 40 \mu\text{A}$$

- Small-signal resistance
  - As far as small changes in the diode current and voltage are concerned, the device behaves as a linear resistor.

$$r_d = \frac{V_T}{I_D}$$

# Example 3.19

---

- When the small change in the diode voltage is time-varying,
  - What happens?

$$I_{D2} = I_s \exp \frac{V_{D1} + \Delta V}{V_T} = I_s \exp \frac{V_{D1}}{V_T} \exp \frac{\Delta V}{V_T}$$

$$I_{D2} \approx I_{D1} \left( 1 + \frac{\Delta V}{V_T} \right)$$

$$I_{D2} = I_s \exp \frac{V_{D1} + \Delta V \cos \omega t}{V_T} = I_s \exp \frac{V_{D1}}{V_T} \exp \frac{\Delta V \cos \omega t}{V_T}$$

$$I_{D2} \approx I_{D1} \left( 1 + \frac{\Delta V \cos \omega t}{V_T} \right)$$