

---

# Lecture16: CMOS amplifier, common-source (3)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# Review


---

- Voltage gain of a common-source amplifier
  - It is given by  $A_v = -g_m(R_D || r_O)$ .
  - By using a current source, we can maximize the voltage gain.
- Rule to calculate the input/output impedances
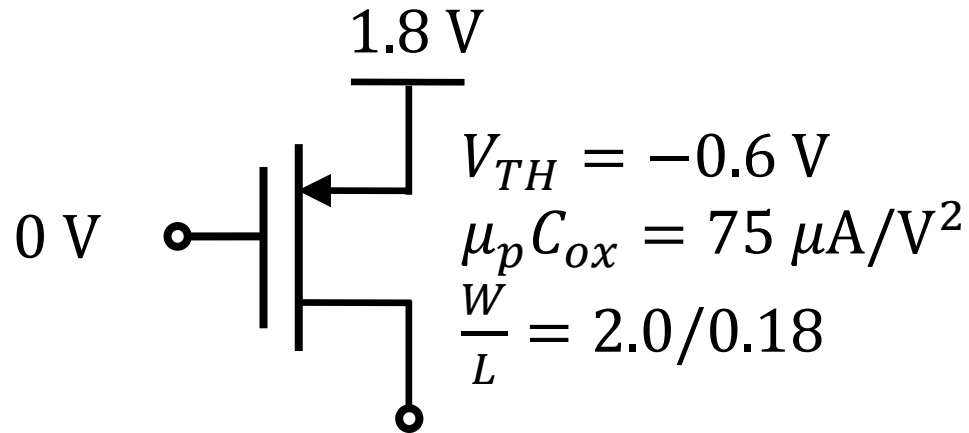
# Biasing of PMOS devices

---

- Use a PMOS as a current source
  - The amount of “gate overdrive” is 1.2 V.
  - It is not 0.6 V.




# Real current-source load

---

- Use a PMOS as a current source.
  - It is not an ideal current source.

$$v_{out} = -g_{m1}(r_{O1}||r_{O2})v_{in}$$


$$A_v = -g_{m1}(r_{O1}||r_{O2})$$

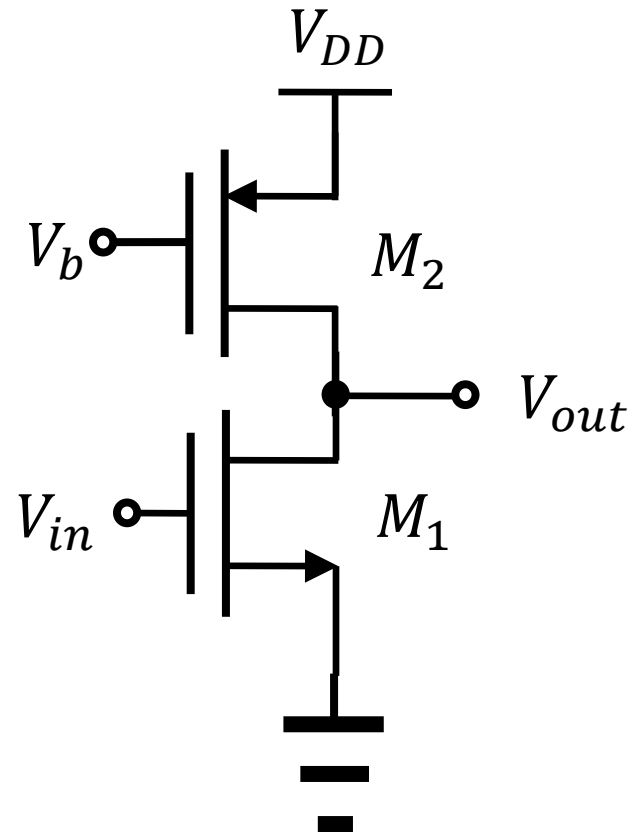
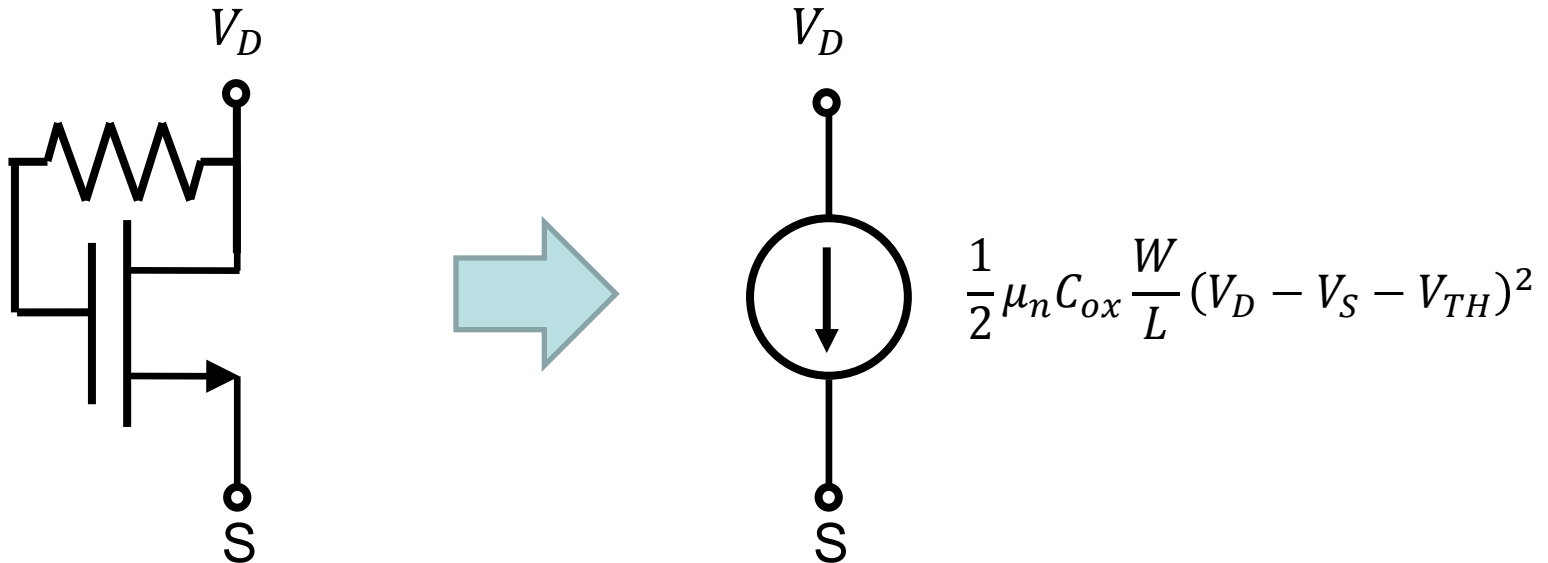
# Self-biasing

---

- Already covered in Example 6.13.
  - Always in the saturation region.



Gate and drain are tied.


# Diode-connected load

---

- Use a diode-connected load.
  - It is not an ideal current source.

$$v_{out} = -g_{m1} \left( r_{O1} \parallel \frac{1}{g_{m2}} \parallel r_{O2} \right) v_{in}$$

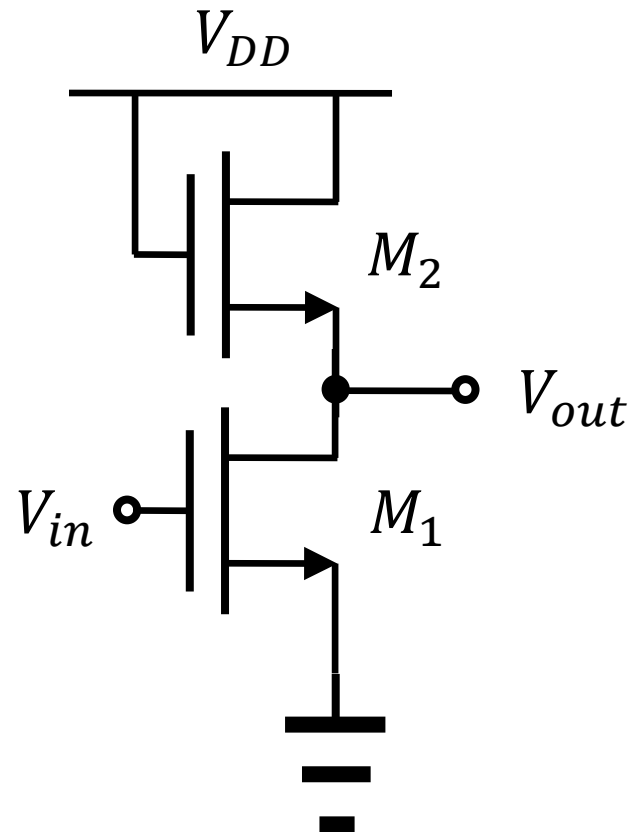
$$A_v = -g_{m1} \left( r_{O1} \parallel \frac{1}{g_{m2}} \parallel r_{O2} \right)$$


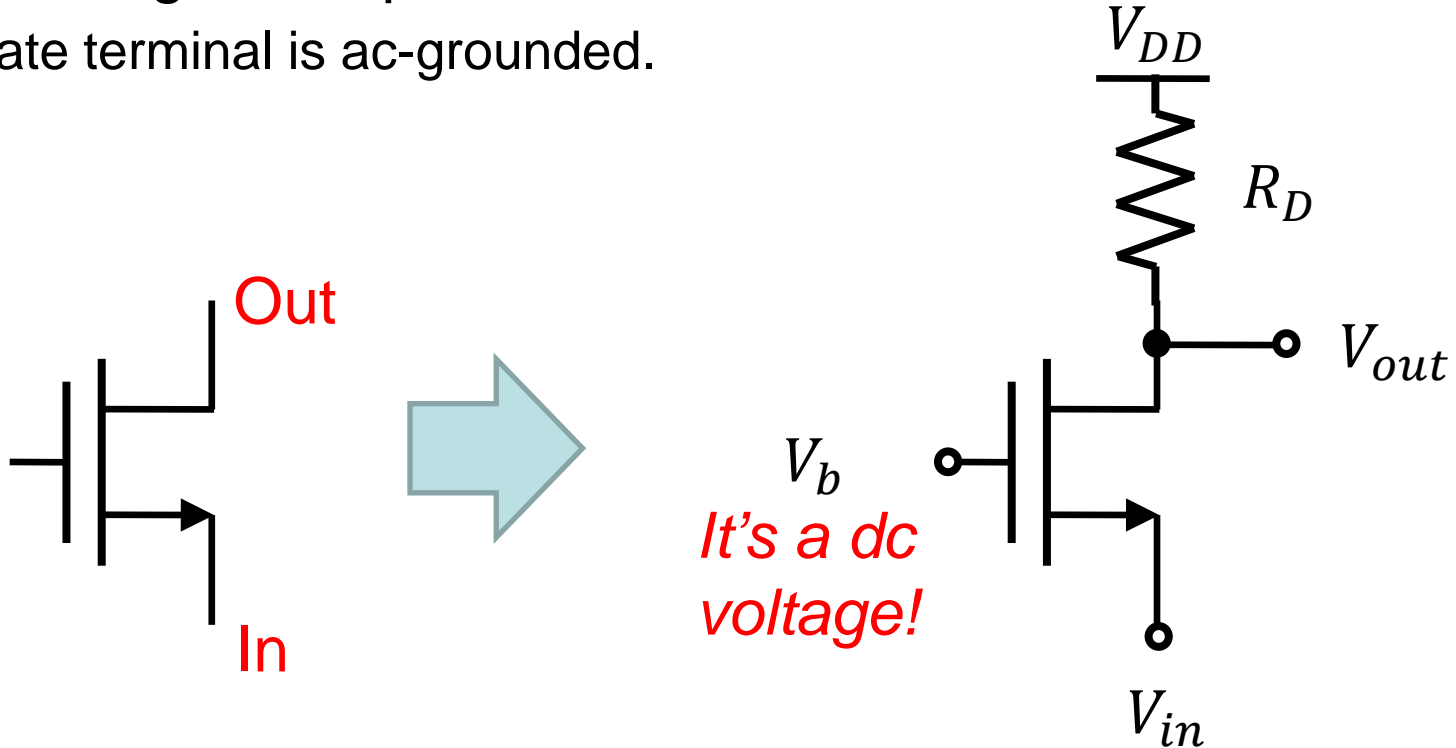
# Common-gate amplifier


---

- Why do we study other amplification topologies?
  - Different circuit properties
- Common-gate amplifier
  - Gate terminal is ac-grounded.


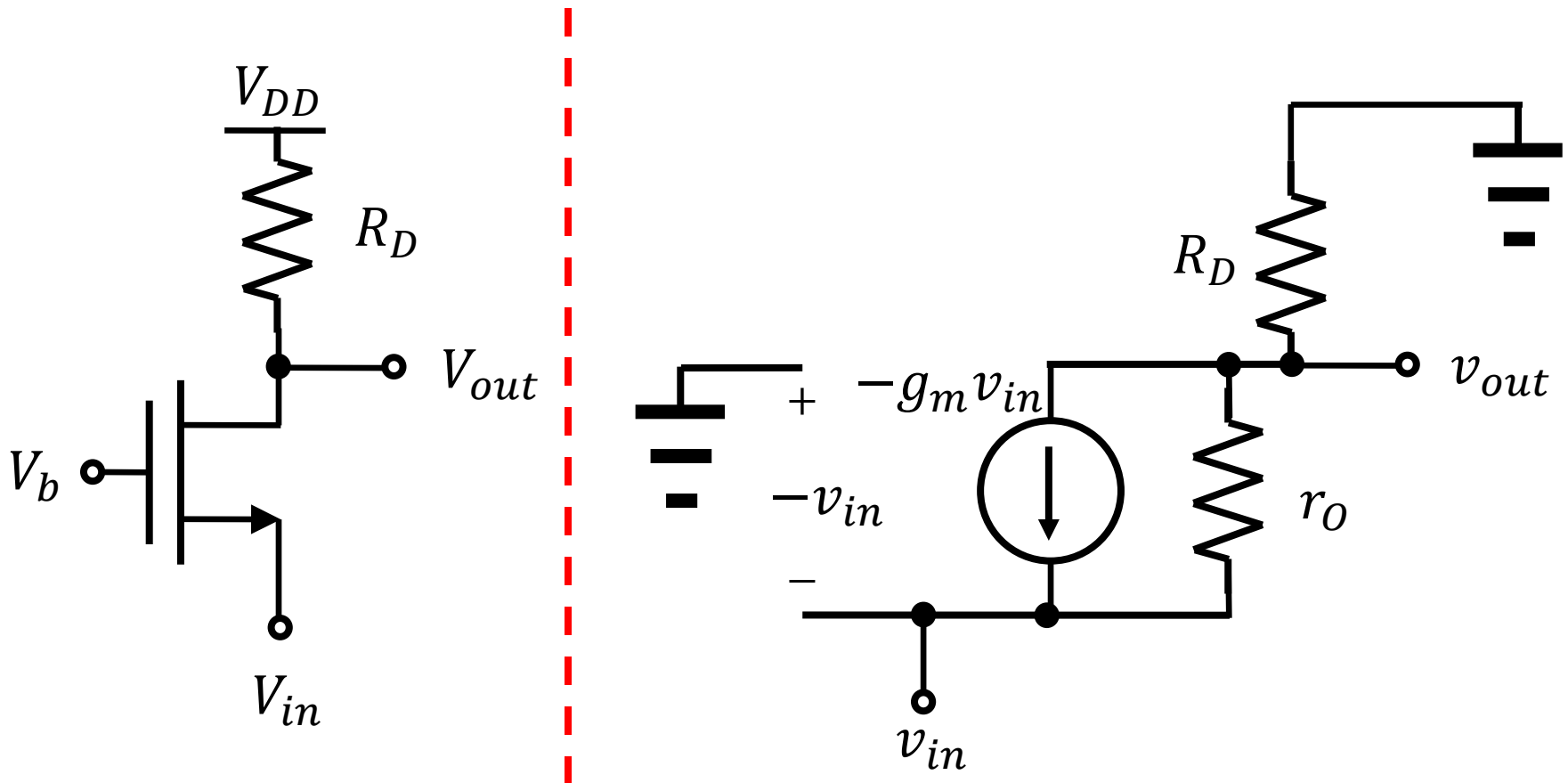
# Small-signal model

- Let's draw the small-signal model together!





# Gain and input impedance

- Neglect the output resistance,  $r_o$ .


- Voltage gain

$$A_v = +g_m R_D$$

- Input impedance

$$R_{in} = \frac{1}{g_m}$$


*It's small!*

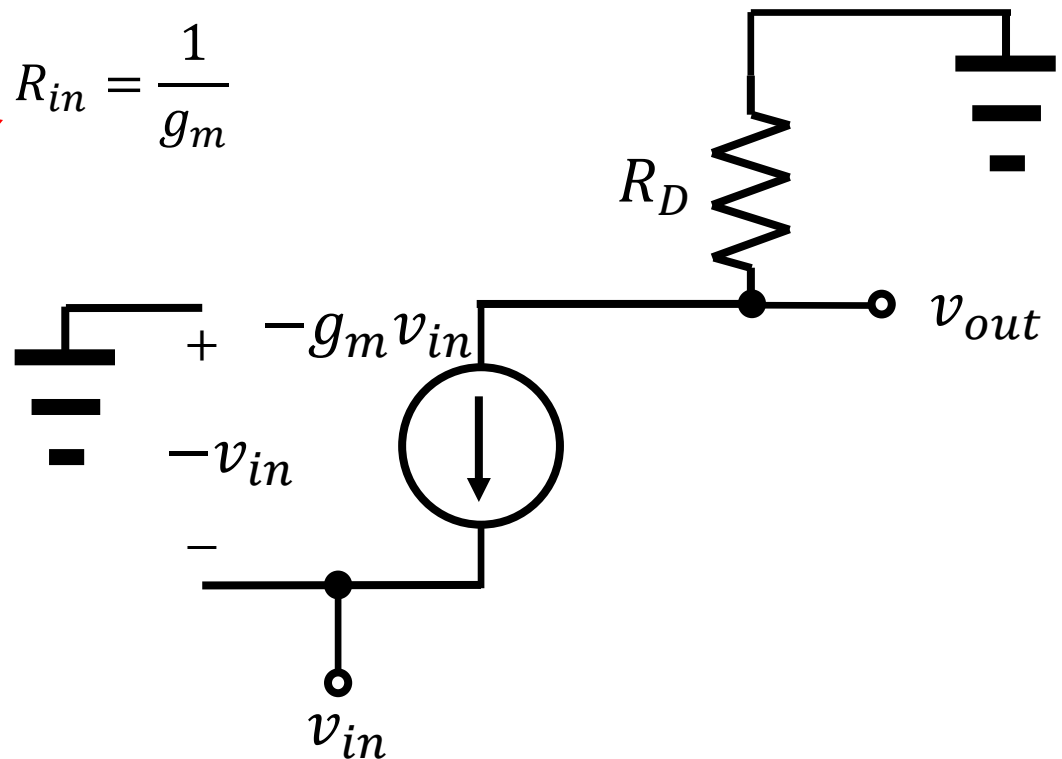


# Output impedance

- Same with the CS stage

$$R_{out} = r_o \parallel R_D$$

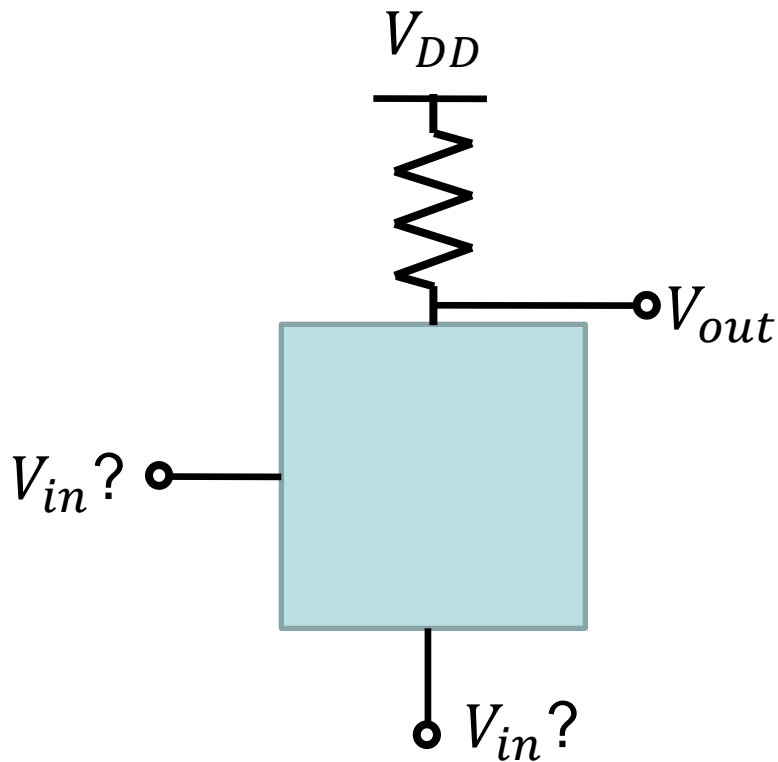

Generic form of CS and CG stages



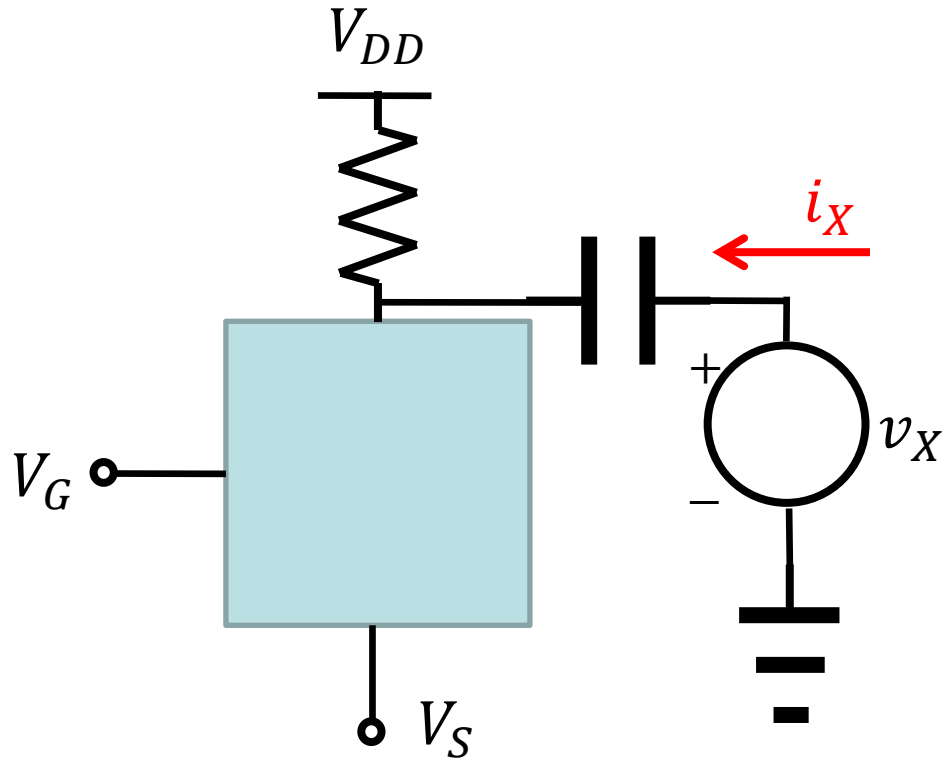


Setting for calculating  $R_{out}$
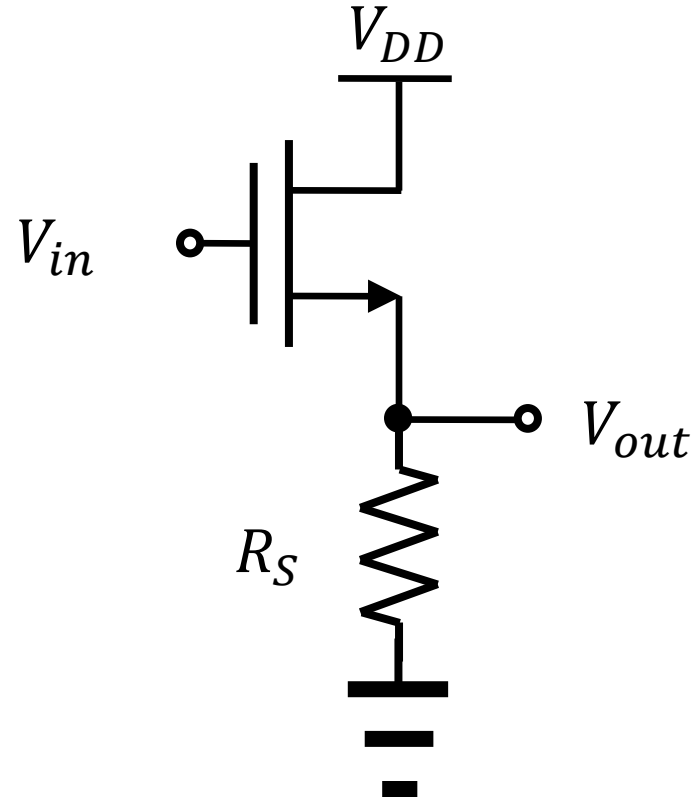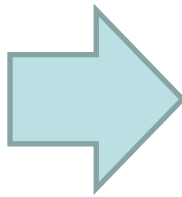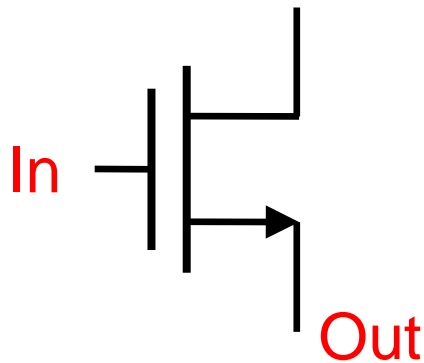
# Source follower

---

- Also called the “common-drain” stage
  - The drain is ac ground.
- Wait a minute!
  - Is it a real amplifier?




# Its core

---

- Gain is less than 1??

$$A_v = + \frac{g_m R_S}{1 + g_m R_S}$$

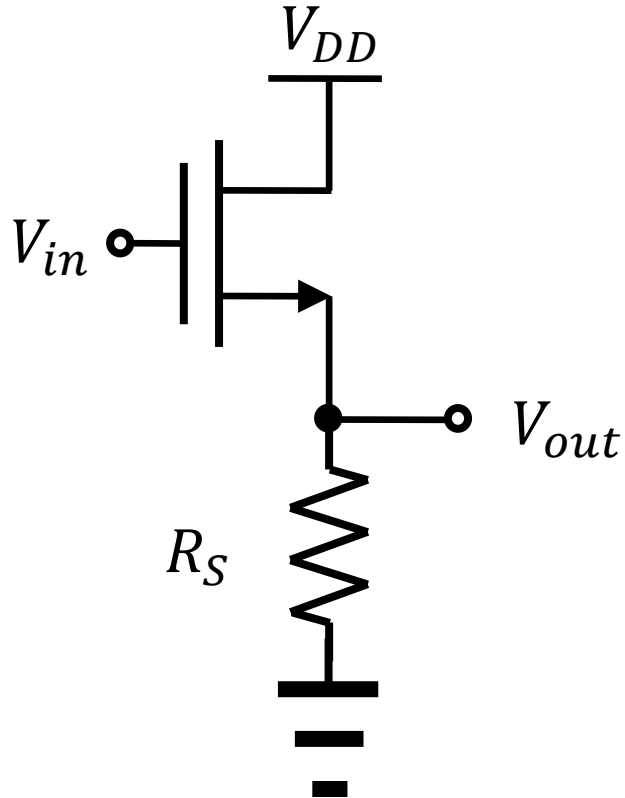

*You should be able to draw the small-signal model.*

# Useless?

---

- Calculate the input and output impedances.
  - Since the gate is the input terminal, the input impedance is very high at low frequencies.
  - How about the output impedance?

$$R_{out} = \frac{1}{g_m} || r_o || R_S$$

- It is relatively low.
- High input imp., low output imp.
  - They can serve as good “buffers.”

